
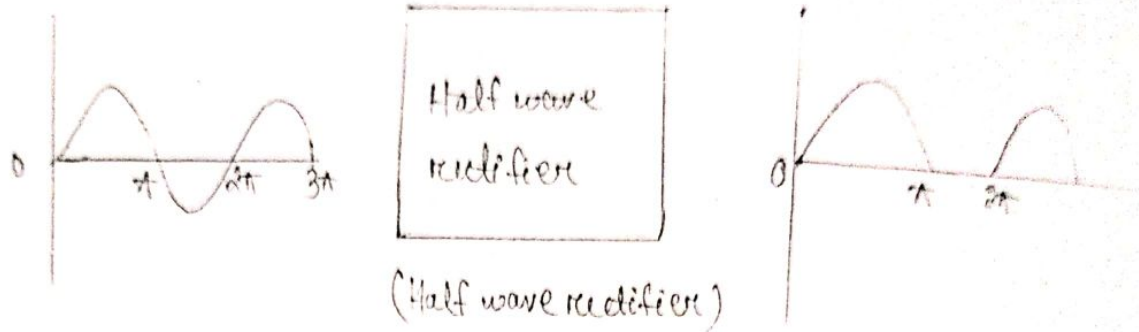


Rectifiers:-

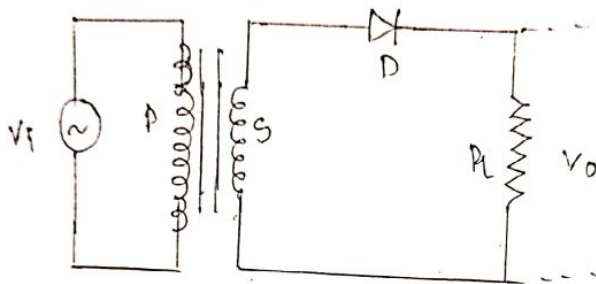A rectifier is defined as an electronic device used in converting A.C voltage or current in unidirectional voltage or current (D.C).



Halfwave Rectifier:-



Analysis:-

→ Let a sinusoidal voltage  $v_i$  be applied to the <sup>input of the</sup> rectifier

then  $v_i = V_m \sin \omega t$ .

→ where,  $V_m = \text{max}^m$  value of supply voltage

→ let the diode be idealized with resistance  $R_f$  in forward direction i.e in on-state

$R_r = \infty$  in the reverse direction in the off-state.

→ now current  $I$  in the diode in the load resistor ( $R_L$ )

$$I = I_m \sin \omega t$$

where  $I_m = \frac{V_m}{R_f + R_L}$

18.12

DC output current & voltages

(i) The average current  $I_{dc}$  is given by  
$$I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i d(\omega t)$$

we know,  $i = I_m \sin \omega t$

$$= \frac{1}{2\pi} \int_0^{2\pi} I_m \sin \omega t d(\omega t)$$

$$= \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t + \frac{1}{2\pi} \int_{\pi}^{2\pi} I_m \sin \omega t d(\omega t)$$

$$= \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t + 0 \quad (\because I_m \sin \omega t d(\omega t) = 0 \text{ when } \pi \text{ to } 2\pi)$$

$$= \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t d(\omega t)$$

$$= \frac{I_m}{2\pi} \left[ -\cos \omega t \right]_0^{\pi}$$

$$= \frac{I_m}{2\pi} \left[ (-\cos \pi) - (-\cos 0) \right]$$

$$= \frac{I_m}{2\pi} \left[ -(-1) - (-1) \right]$$

$$= \frac{I_m}{2\pi} (-(-2))$$

$$= \frac{I_m}{2\pi} \times 2 = \frac{I_m}{\pi}$$

$$= 0.318 I_m$$

$$\boxed{I_{dc} = \frac{I_m}{\pi} = 0.318 I_m} \quad \because \frac{1}{\pi} = 0.318$$

Substituting the value of  $I_m$

$$\boxed{I_{dc} = 0.318 \frac{V_m}{R_f + R_L}}$$

11.8

(ii) DC

(iii) Root  
RMS  
=  $\frac{I_m}{\sqrt{2}}$

$$I_{dc} = \frac{V_m}{\pi(R_f + R_L)}$$

If  $R_f \ll R_L$  then

$$I_{dc} = \frac{V_m}{\pi(0 + R_L)}$$

$$\Rightarrow I_{dc} = \frac{V_m}{0 + \pi R_L}$$

$$\Rightarrow I_{dc} = \frac{V_m}{\pi R_L}$$

(ii) DC output voltage  $V_{dc} = I_{dc} \times R_L$

$$= \frac{V_m}{\pi R_L} \times R_L$$

$$= \frac{V_m}{\pi}$$

$$V_{dc} = \frac{V_m}{\pi} = 0.318 V_m$$

Root mean square

(iii) RMS current & voltage:-

The value of RMS current is given by

$$I_{rms} = \left[ \frac{1}{2\pi} \int_0^{2\pi} i^2 d(\omega t) \right]^{1/2}$$

$$= \left[ \frac{1}{2\pi} \int_0^{2\pi} i^2 d(\omega t) \right]^{1/2}$$

$$= \left[ \frac{1}{2\pi} \int_0^{\pi} (I_m \sin(\omega t))^2 d(\omega t) + \int_{\pi}^{2\pi} 0 \cdot d(\omega t) \right]^{1/2}$$

$$= \left[ \frac{1}{2\pi} \int_0^{\pi} I_m^2 \sin^2(\omega t) d(\omega t) \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{2\pi} \cdot \left( \frac{1 - \cos 2\omega t}{2} \right) d(\omega t) \right]^{1/2} \quad (\because \sin^2 \theta = \frac{1 - \cos 2\theta}{2})$$

$$= \left[ \frac{I_m^2}{2\pi} \int_0^{\pi} \left( \frac{1}{2} - \frac{\cos 2\omega t}{2} \right) d(\omega t) \right]^{1/2}$$

$i(\omega t) = 0$   
at  $2\pi$

$$\begin{aligned}
 &= \left[ \frac{I_m^2}{2\pi} \int_0^\pi \left( \frac{1}{2} - \frac{\cos 2\omega t}{2} \right) d(\omega t) \right]^{1/2} \\
 &= \left[ \frac{I_m^2}{2\pi} \left[ \frac{1}{2} \omega t - \frac{1}{2} \times \frac{\sin 2\omega t}{2} \right]_0^\pi \right]^{1/2} \\
 &= \left[ \frac{I_m^2}{4\pi} \left[ \omega t - \frac{\sin \omega t}{2} \right]_0^\pi \right]^{1/2} \\
 &= \left[ \frac{I_m^2}{4\pi} \left( \pi - 0 - \left( \frac{\sin 2\pi}{2} - \sin 0 \right) \right) \right]^{1/2} \\
 &= \left[ \frac{I_m^2}{4\pi} \times \pi \right]^{1/2}
 \end{aligned}$$

$$I_{RMS} = \sqrt{\frac{I_m^2}{4}} = \frac{I_m}{2}$$

Substituting the value of  $I_m$

$$I_{RMS} = \frac{V_m}{R_f + R_s}$$

$$\Rightarrow I_{RMS} = \frac{V_m}{2(R_f + R_s)}$$

If  $R_f \ll R_s$

$$I_{RMS} = \frac{V_m}{2(0 + R_s)}$$

$$\Rightarrow I_{RMS} = \frac{V_m}{2R_s}$$

RMS voltage

$$\begin{aligned}
 V_{RMS} &= I_{RMS} \times R_s \\
 &= \frac{V_m}{2} \times R_s \\
 &= \frac{V_m}{2} \times R_s
 \end{aligned}$$

$$R_f \ll R_s = \frac{V_m \times R_s}{2R_s} \quad \therefore$$

$$\Rightarrow \boxed{V_{RMS} = \frac{V_m}{2}}$$

RES

→

out

func

Par

## RECTIFIER EFFICIENCY:-

D-16-8-17 15

The rectifier efficiency is defined as ratio of dc output power to ac input power.

$$\eta = \frac{\text{dc power delivered to load}}{\text{a.c input power}} = \frac{P_{dc}}{P_{ac}}$$

$$\begin{aligned} P_{dc} &= (I_{dc})^2 \cdot R_L \\ &= \left(\frac{I_m}{\pi}\right)^2 \cdot R_L \\ &= \frac{I_m^2}{\pi^2} \cdot R_L \end{aligned}$$

further  $P_{ac} = P_a + P_r$

where,  $P_a$  = power dissipated at the junction diode

$$\begin{aligned} P_a &= (I_{rms})^2 \cdot R_f \\ &= \left(\frac{I_m}{\sqrt{2}}\right)^2 \cdot R_f \\ &= \frac{I_m^2}{4} R_f \end{aligned}$$

$P_r$  = power dissipated by the load resistance.

$$\begin{aligned} P_r &= (I_{rms})^2 \cdot R_L \\ &= \left(\frac{I_m}{\sqrt{2}}\right)^2 \cdot R_L \\ &= \frac{I_m^2}{4} \cdot R_L \end{aligned}$$

$$\begin{aligned} P_{ac} &= P_a + P_r \\ &= \frac{I_m^2}{4} \cdot R_f + \frac{I_m^2}{4} \cdot R_L \\ &= \frac{I_m^2}{4} (R_f + R_L) \end{aligned}$$

$$\eta = \frac{\frac{I_m^2}{4} \cdot R_L}{\frac{I_m^2}{4} (R_f + R_L)} = \frac{I_m^2 \cdot R_L}{I_m^2 (R_f + R_L)}$$

$$= \frac{4 I_m^2 \cdot R_L}{4 I_m^2 (R_f + R_L)}$$

$$\eta = 0.406 \times \frac{R_L}{(R_f + R_L)}$$

When,  $R_f \ll R_L$

$$\eta = 40.6\%$$

### RIPPLE FACTOR:-

→ The output of a rectifier consists of dc component as well as  
 1. The d.c component in the output called rectifier this is undesired.

→ Smaller is the ripple more effective will be the rectifier.

→ The ripple factor ( $\gamma$ ) give an idea about the waviness of the rectifier voltage and it is defined as ratio of effective value of a.c component of voltage.

$$\text{Ripple factor } (\gamma) = \frac{\text{Ripple voltage}}{\text{D.C voltage}}$$

$$= \frac{\text{Rms value of a.c component } (V_{ac})_{\text{RMS}}}{\text{D.C value of wave } V_{dc}}$$

$(V_r)_{rms}$  = rms value of a.c component of o/p voltage

$V_{dc}$  = d.c value of o/p component

$$(V_r)_{rms}^2 = (V_{rms})^2 - V_{dc}^2$$

$$\Rightarrow (V_r)_{rms} = \sqrt{V_{rms}^2 - V_{dc}^2}$$

$$\text{Ripple factor} = \frac{\sqrt{V_{rms}^2 - V_{dc}^2}}{V_{dc}} = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

$$= \sqrt{\frac{V_{rms}^2 - V_{dc}^2}{V_{dc}^2}} = \sqrt{\frac{\left(\frac{V_m}{\sqrt{2}}\right)^2}{\left(\frac{V_m}{\sqrt{2}}\right)^2} - 1}$$

$$= \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1} = \sqrt{\frac{\pi^2}{8} - 1} = 1.21$$

The ripple factor also defined as

$$\text{Ripple factor} = \frac{I_{rms}}{I_{dc}} = \frac{(I_r)_{rms}}{I_{dc}}$$

### REGULATION:-

It is defined as the variation of d.c o/p voltage with change in d.c ~~out~~ load current.

$$\% \text{ of Regulation} = \frac{V_{no\ load} - V_{full\ load}}{V_{full\ load}} \times 100$$

### TRANSFORMER UTILIZATION FACTOR:-

The d.c power to be delivered to the load in a rectifier circuit decides the rating of the transformer used in the circuit. So transformer utilization factor is defined as.

$$\text{TUF} = \frac{\text{d.c power to be delivered to the load}}{\text{Ac rating to the transformer secondary}} = \frac{P_{dc}}{(P_r)_{transformer}}$$

D-18.8.18

According to theory of transformer the rated of secondary will be  $\frac{V_m}{\sqrt{2}}$  and the actual rms current flowing through it will be  $\frac{I_m}{2}$ .

$$\begin{aligned} \text{TUF} &= \frac{P_{dc}}{P_{ac \text{ rated}}} \\ &= \frac{(I_{dc})^2 R_L}{V_a \times I_{rms}} \\ &= \frac{\left(\frac{I_m}{2}\right)^2 \times R_L}{\frac{V_m}{\sqrt{2}} \times \frac{I_m}{2}} \\ &= \frac{I_m^2 \times R_L}{4} \\ &= \frac{V_m \cdot I_m}{2\sqrt{2}} \\ &= \frac{I_m^2 \times R_L \times 2\sqrt{2}}{4 \times V_m \times I_m} \end{aligned}$$

we know  $V_m = I_m (R_f + R_L)$

$$\frac{I_m^2 \times R_L \times 2\sqrt{2}}{4 I_m^2 (R_f + R_L)}$$

$$\text{TUF} = \frac{2\sqrt{2}}{4} \frac{R_L}{R_f + R_L}$$

when  $R_f \ll R_L$   $\frac{2\sqrt{2}}{4} \left( \frac{R_L}{0 + R_L} \right)$

$$= \frac{2\sqrt{2}}{4} \left( \frac{R_L}{R_L} \right)$$

$$= \frac{2\sqrt{2}}{4} = 0.707$$



This means that if the transformer rating is  $2 \text{ kVA} \frac{12}{1}$   
 $1000 \text{ V} \cdot \text{A}$  then half wave rectifier can deliver  
 $1000 \times 0.287 = 287 \text{ watt}$  to the resistance load.

### Peak inverse voltage (PIV) :-

The peak inverse voltage (PIV) is defined as the  
 max<sup>m</sup> voltage across the diode in the reverse direction

$$\text{PIV} = V_m$$

### Form Factor (F) :-

It is defined as the ratio of rms value of  
 current to the ~~ratio~~ average value of the current

$$\begin{aligned} F &= \frac{I_{\text{rms}}}{I_{\text{avg}}} \\ &= \frac{I_m/2}{\frac{I_m \cdot \pi}{2\pi}} \\ &= \frac{I_m \cdot \pi}{I_m \cdot 2} \end{aligned}$$

$$= \pi/2 = 1.57$$

### Peak Factor :-

It is defined as the ratio of peak value to the  
 rms value of voltage.

$$\text{Peak Factor} = \frac{V_{\text{peak}}}{V_{\text{rms}}}$$

$$= \frac{V_m}{\frac{V_m}{2}}$$

$$= 2$$

Q:- In the power supply dc output <sup>voltage</sup> drop from 44V with no load to 42V at a full load what is the % of regulation.

$$\begin{aligned} \% \text{ of regulation} &= \frac{V_{\text{no load}} - V_{\text{full load}}}{V_{\text{full load}}} \times 100 \\ &= \frac{44 - 42}{42} \times 100 = 0.0476 \times 100 = 4.76\% \end{aligned}$$

Q:- What is ripple 2V on avg of 50V ~~what is~~:

$$\begin{aligned} \text{Ripple} &= 2 \\ \text{Avg} &= 50 \\ \text{Ripple} &= \frac{2}{50} = 0.04 \end{aligned}$$

Q:- An ac supply of 230V is applied to a half wave rectifier circuit through transformer of turns ratio 5:1 assume the diode is an ideal one.

The load resistance is 300Ω.

Find (i) DC output voltage

(ii) PIV

(iii) Max<sup>m</sup> value power deliver to the load

(iv) The avg. value of power deliver to the load.

$$\frac{V_2}{V_1} = \frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$\rightarrow \frac{230}{5} = 46$$

$$V_m = 46 \times \sqrt{2} = 65$$

$$V_{dc} = \frac{V_m}{\pi} = \frac{65}{\pi} = 20.7$$

$$PIV = V_m = 65V$$

$$V_m = I_m (R_f + R_L)$$

$$\frac{V_m}{R} = I_m$$

$$I_m = \frac{65}{300} = 0.217 \text{ Amp}$$

$$\begin{aligned} P_m &= I_m^2 \times R_L \\ &= (0.217)^2 \times 300 = 14.12 \end{aligned}$$

$$I_{dc} = \frac{0.217}{3.142} = 0.069$$

$$\begin{aligned} P_{dc} &= (I_{dc})^2 \times R_L \\ &= (0.069)^2 \times 300 = 1.428 \end{aligned}$$

18

D-20.8.18

A sinusoidal voltage of amplitude 25V & freq. 50 Hz is applied to a halfwave rectifier the load resistor is 1000Ω the forward resistance  $R_f$  of ideal diode is 10Ω. Calculate peak average, and rms value of current, dc power output, rectifier  $\eta$ , ripple factor.

$$V_m = 25V$$

$$I_m = \frac{V_m}{R_f + R_L} = \frac{25}{10 + 1000} = 0.02475 \text{ amp} = 24.75 \text{ mA}$$

$$I_{dc} = \frac{I_m}{\pi} = 7.87 \text{ mA}$$

$$I_{rms} = \frac{I_m}{2} = \frac{24.75}{2} = 12.37 \text{ mA}$$

$$P_{dc} = I_{dc}^2 \times R_L$$

$$= (7.87)^2 \times 1000$$

$$= 61.9 \text{ mW}$$

$$P_{ac} = I_{rms}^2 (R_f + R_L)$$

$$= \left( \frac{12.37}{1000} \right)^2 \times (10 + 1000)$$

$$= 154.53 \text{ mW}$$

$$\eta = \frac{P_{dc}}{P_{ac}} \times 100$$

$$= \frac{61.9}{154.53} \times 100$$


$$= 40\%$$

$$\text{Ripple factor} = \frac{(I_{rms})_{ac}}{I_{dc}}$$


$$= \sqrt{\left( \frac{I_{rms}}{I_{dc}} \right)^2 - 1} = \sqrt{\left( \frac{12.37}{7.87} \right)^2 - 1}$$

$$= 1.21$$

## Full-wave Rectifier:-

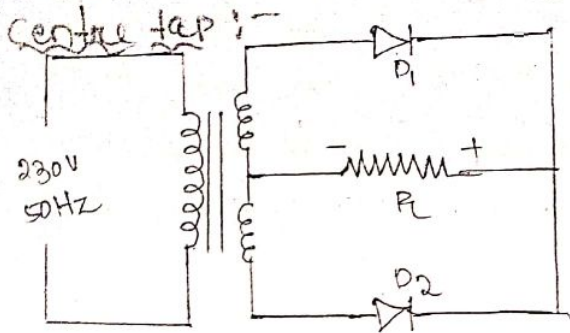



$V_{out}$

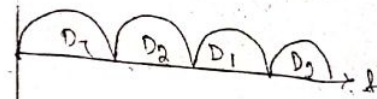

Similarly

$R = 28$

## Bridge Rectifier:-

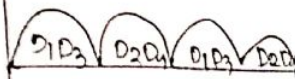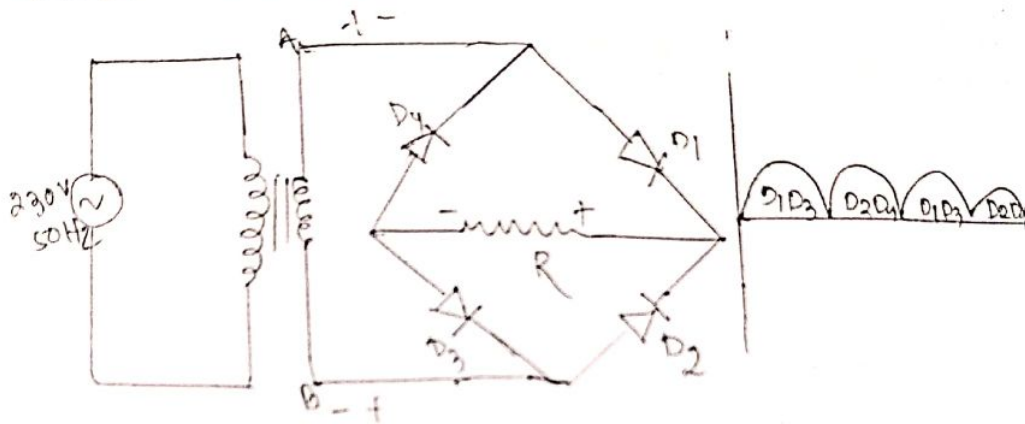

The total

current

DC 0

for +ve

$D_1$  &  $D_3$  forward bias

$D_2$  &  $D_4$  R.B

for -ve

$D_1$  &  $D_3$  Reverse bias

$D_2$  &  $D_4$  forward bias

Analysis -

Let the input voltage  $V_e$  is given by  $V_e = V_m \sin \omega t$

The current  $i_1$  through diode  $D_1$  & load resistor is given by  $i_1 = I_m \sin \omega t$ , for  $0 \leq \omega t \leq \pi$

$i_1 = 0$ , for  $\pi \leq \omega t \leq 2\pi$

$$I_m = \frac{V_m}{2R + R}$$


Where,  $R_L$  = load resistance  $R_L$  on conductor 19

Similarly,  
The current  $i_2$  flowing to diode  $D_2$  of load resistor  $R_L$  is given by,

$$i_2 = 0 \text{ for } \omega t < \pi$$

$$i_2 = I_m \sin \omega t \text{ for } \pi \leq \omega t < 2\pi$$

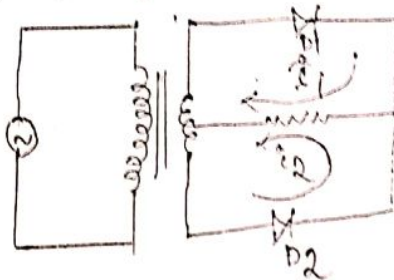The total current flowing through the  $R_L$  is the sum of the current  $i_1$  &  $i_2$  i.e.  $i = i_1 + i_2$



DC or Average current:

$$I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i(\omega t) d(\omega t)$$

$$\Rightarrow I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i_1 + i_2 d(\omega t)$$

$$\Rightarrow I_{dc} = \frac{1}{2\pi} \left[ \int_0^{\pi} i_1 d(\omega t) + \int_{\pi}^{2\pi} i_2 d(\omega t) \right]$$

$$= \frac{1}{2\pi} \left[ \int_0^{\pi} I_m \sin \omega t d(\omega t) + \int_{\pi}^{2\pi} I_m \sin \omega t d(\omega t) \right]$$

$$= \frac{1}{2\pi} \left[ I_m (-\cos \omega t) \Big|_0^{\pi} \right] + \frac{1}{2\pi} \left[ I_m (-\cos \omega t) \Big|_{\pi}^{2\pi} \right]$$

$$= \frac{1}{2\pi} \left[ I_m (-1 - (-1)) \right] + \frac{1}{2\pi} \left[ I_m (-1 - (-1)) \right]$$

$$= \frac{1}{2\pi} [2I_m] + \frac{1}{2\pi} [2I_m]$$

$$= \frac{I_m}{\pi} + \frac{I_m}{\pi}$$

$$I_{dc} = \frac{2I_m}{\pi} = 0.636 I_m$$

$$V_{dc} = I_{dc} \times R$$

$$= \frac{2I_m}{\pi} \times R$$

$$\boxed{V_{dc} = 0.636 I_m R}$$

$$\text{D} = 23.8\%$$

RMS current:

The rms value of current is given by,

$$I_{rms} = \left[ \frac{1}{T} \int_0^T i^2 dt \right]^{1/2}$$

$$= \left[ \frac{1}{T} \int_0^T I_m^2 \sin^2(\omega t) dt \right]^{1/2} \quad \left( \text{since, current is of the same form in the two halves} \right)$$

$$= \left[ \frac{I_m^2}{T} \int_0^T \sin^2(\omega t) dt \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{T} \int_0^T \frac{1 - \cos 2\omega t}{2} dt \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{2T} \left( \int_0^T dt - \int_0^T \cos 2\omega t dt \right) \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{2T} \left( (t) - \frac{\sin 2\omega t}{2} \right) \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{2T} (T - 0 - 0 - 0) \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{2} \right]^{1/2}$$

$$= \left[ \frac{I_m^2}{2} \right]^{1/2}$$

$$\boxed{I_{rms} = \sqrt{\frac{I_m^2}{2}} = \frac{I_m}{\sqrt{2}}$$

RMS voltage:

$$V_{rms} = I_{rms} \times R$$

$$= \frac{V_m}{\sqrt{2}} \times R$$

$$\left( \because I_m = \frac{V_m}{R+R} \text{ ; } I_{rms} = \frac{I_m}{\sqrt{2}} \right)$$

If  $R_1 \neq R_2$

$$\boxed{V_{rms} = \frac{V_m R}{\sqrt{2}(R_1+R_2)} = \frac{V_m \times R}{\sqrt{2} R} = \frac{V_m}{\sqrt{2}}$$

## Rectifier efficiency for full wave:-

20

$$\eta = \frac{P_{dc}}{P_{ac}}$$

$$P_{dc} = I_{dc}^2 R$$
$$= \frac{V_{dc}^2}{R}$$

$$= \frac{4V_m^2}{\pi^2 R} \quad \left( \because V_{dc} = \frac{2V_m}{\pi} \right)$$

$$P_{ac} = I_{rms}^2 R$$

$$= \frac{V_{rms}^2}{R} = \frac{(V_m/\sqrt{2})^2}{R} = \frac{V_m^2}{2R}$$

$$\eta = \frac{4V_m^2}{\pi^2 R} \cdot \frac{2R}{V_m^2}$$

$$= \frac{4V_m^2}{\pi^2 R} \cdot \frac{2R}{V_m^2} = \frac{8}{\pi^2} = 0.812 = 81.2\%$$

## Ripple factor:-

$$r = \sqrt{\left( \frac{I_{rms}}{I_{dc}} \right)^2 - 1}$$

$$= \sqrt{\left( \frac{\frac{I_m}{\sqrt{2}}}{\frac{2I_m}{\pi}} \right)^2 - 1} = \sqrt{\left( \frac{\pi}{2\sqrt{2}} \right)^2 - 1}$$

$$= \sqrt{\frac{\pi^2}{8} - 1} = 0.48$$

## Regulation:-

The dc output voltage is given by,  $V_{dc} = \frac{2I_m \cdot R}{\pi}$

$$V_{dc} = \frac{2I_m \cdot R}{\pi}$$

$$= \frac{2V_m R}{\pi (R_f + R_c)} \quad \left( \because I_m = \frac{V_m}{R_f + R_c} \right)$$

$$= \frac{2V_m}{\pi} \left( 1 - \frac{R_f}{R_f + R_c} \right) = \frac{2V_m}{\pi} - \frac{2V_m}{\pi} \cdot \frac{R_f}{R_f + R_c}$$

$$= \frac{2V_m}{\pi} - I_{dc} \cdot R_f$$

Peak Inverse Voltage:

→ The peak inverse voltage is the max<sup>n</sup> possible voltage across a diode when it is reverse biased.

→ In centre tap full wave rectifier the peak inverse voltage =

$$V_m + V_m = 2V_m$$

→ In bridge full wave rectifier the peak inverse voltage

is  $V_m$

D-26.8.18

Transformer utilisation factor (TUF): - (Full wave centre tap)

→ The average TUF in full wave rectifying circuit is determined by considering the primary and secondary winding separately

→ There are two secondary's here, each secondary is associated with one diode that is just similar to secondary of half wave rectifier.

→ Each secondary has TUF of 0.884

TUF of primary: -

$$\text{TUF of primary} = \frac{P_{ac}}{V-I \text{ rating of primary}}$$

$$= \frac{(I_{dc})^2 R_L}{V_{rms} \times I_{rms}}$$

$$= \frac{\left(\frac{2I_m}{\pi}\right)^2 R_L}{\frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}}}$$

$$= \frac{4I_m^2 R_L \times \sqrt{2} \times \sqrt{2}}{\pi^2 \times V_m \times I_m} = \frac{8I_m^2 R_L}{I_m^2 (R_f + R) \pi^2}$$

$$= \frac{8R_L}{\pi^2 (R_f + R)}$$

When  $R_f \ll R$

$$= \frac{8R_L}{\pi^2 R} = \frac{8}{\pi^2} = 0.810$$



$$(TUF)_{avg} = \frac{(TUF)_p + 0.287 + 0.287}{2}$$

$$= 0.692$$

Form factor:-

$$F = \frac{I_{rms}}{I_{dc}} = \frac{I_m/\sqrt{2}}{2I_m/\pi}$$

$$= \frac{I_m \times \pi}{\sqrt{2} I_m}$$

$$= \pi/\sqrt{2} = 1.110$$

Peak factor:-

$$PF = \frac{V_{peak}}{I_{rms}}$$

Comparison bet<sup>n</sup> half wave rectifier with full wave rectifier.

<u>Terms</u>	<u>halfwave</u>	<u>fullwave</u>
Avg or dc value of current ( $I_{dc}$ )	$\frac{I_m}{\pi}$	$\frac{2I_m}{\pi}$
Avg or dc value of voltage ( $V_{dc}$ )	$\frac{V_m}{\pi}$	$\frac{2V_m}{\pi}$
RMS current ( $I_{rms}$ )	$\frac{I_m}{2}$	$\frac{I_m}{\sqrt{2}}$
RMS voltage ( $V_{rms}$ )	$\frac{V_m}{2}$	$\frac{V_m}{\sqrt{2}}$
Efficiency (%)	40.6%	81.2%
Ripple factor	1.21	0.48
PIV	$V_m$	$2V_m$ (Centre tap) $V_m$ (Bridge rectifier)
TUF	0.287	0.692 (Centre tap) 0.812 (Bridge rectifier)
Form factor	1.57	1.110
Peak factor	2	$\sqrt{2}$

TUF (bridge):- The transformer utilization factor TUF the primary & secondary will <sup>be</sup> same as the ~~freq~~ ~~is~~ always current through primary & secondary.

$$\frac{(TUF)_p + (TUF)_s}{2} = \frac{0.810 + 0.810}{2} = 0.81$$

D-27.8.19

Q. A full wave rectifier supply a load  $1k\Omega$ . The ac voltage applied to the diode is  $220 - 0 - 220V$  rms. If diode resistance is neglected calculate :- (1) Avg dc voltage

- (2) Avg dc current
- (3) Ripple current

$$(1) V_{dc} = \frac{2V_m}{\pi} = 0.636 V_m$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\begin{aligned} \rightarrow V_m &= V_{rms} \times \sqrt{2} \\ &= 0.636 \times 220 \times \sqrt{2} \\ &= 198V \end{aligned}$$

$$(3) V = \frac{(V_{ic})_{rms}}{V_{dc}}$$

$$\begin{aligned} &= V_{ic} \cdot V_{dc} = (V_{ic})_{rms} \\ &= 0.48 \times 198 = 95.04V \\ &= 99.04V \end{aligned}$$

$$(2) I_{dc} = \frac{V_{dc}}{R_L}$$

$$= \frac{198}{1000} = 0.198 = 198mA$$

Q. The full wave PN diode rectifier uses a load resistor of  $1500\Omega$  no filter is used. Diode to have idealised characteristics with  $R_f = 10\Omega$  and  $R_{ro} = \infty$ . Since the wave voltage applied to the each diode has amplitude of  $30V$  calculate peak, dc rms, load current and dc power o/p, I/P and efficiency.

Given data

$$R_f = 10\Omega$$

$$V_m = 30V$$

$$\begin{aligned} I_m &= \frac{V_m}{R_f + R_L} \\ &= \frac{30}{10 + 1500} \end{aligned}$$

$$= 0.01986 \text{ amp}$$

$$I_{dc} = \frac{2I_m}{\pi}$$

$$= \frac{2 \times 0.01986}{\pi}$$

$$= \frac{2 \times 0.01986}{3.14}$$

$$= 0.01264 \text{ amp}$$

$$\begin{aligned} I_{rms} &= \frac{I_m}{\sqrt{2}} \\ &= \frac{0.01986}{\sqrt{2}} = 0.01404 \text{ amp} \end{aligned}$$

$$\begin{aligned} \text{dc power o/p} &= P_{dc} = (I_{dc})^2 \cdot R_L \\ &= (0.01264)^2 \times 1500 \\ &= 0.23965 \text{ watt} \end{aligned}$$

DC power o/p :-

$$P_{ac} = (I_{rms})^2 \cdot (R_f + R_L)$$

$$= (0.01404)^2 \times (10 + 1500)$$

$$= 0.29765 \text{ watt}$$

$$\text{Efficiency} = \frac{P_{dc}}{P_{ac}} \times 100$$

$$= \frac{0.23965}{0.29765} \times 100$$

$$= 80.51\%$$

$$D = 28.8 \cdot 18$$

22

Q:- A full wave rectifier delivers 50 watt to the load  
2000. If ripple factor is calculate the AC ripple  
voltage across the load.

$$P_{dc} = \frac{V_{dc}^2}{R}$$

$$\rightarrow P_{dc} \times R = V_{dc}^2$$

$$\rightarrow V_{dc} = \sqrt{P_{dc} \times R}$$
$$= \sqrt{50 \times 2000} = 100V$$

$$r = \frac{V_{rms}}{V_{dc}} = \frac{2}{100} \times 100 = 2V$$

Q:- A bridge rectifier is used supply dc load of 20 amp  
and 20 volt. from 117 volt source. what are the rating  
from the power transformer :

$$V_{dc} = 20V$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{dc} = \frac{2V_m}{\pi}$$

$$= \frac{31.4}{\sqrt{2}}$$

$$\rightarrow 20 = \frac{2V_m}{\pi}$$

$$= 22.2 \text{ volt}$$

$$\rightarrow V_m = \frac{20\pi}{2} = 10\pi = 31.4 \text{ volt}$$

$$I_{dc} = \frac{2I_m}{\pi}$$

$$\rightarrow 20 = \frac{2I_m}{\pi}$$

$$\rightarrow I_m = 31.4 \text{ amp}$$

$$I_{rms} = 22.2 \text{ A}$$

$$\frac{V_2}{V_1} = \frac{I_1}{I_2}$$


$$\rightarrow \frac{22.2}{117} = \frac{I_1}{22.2}$$

$$V_{rms} \times I_{rms} = 22.2 \times 22.2$$
$$= 492.84$$



$$\rightarrow I_1 = \frac{22.2 \times 22.2}{117} = 4.21$$

$$V_1 \times I_1 = 117 \times 4.21$$
$$= 492.57$$




# shunt capacitor filters

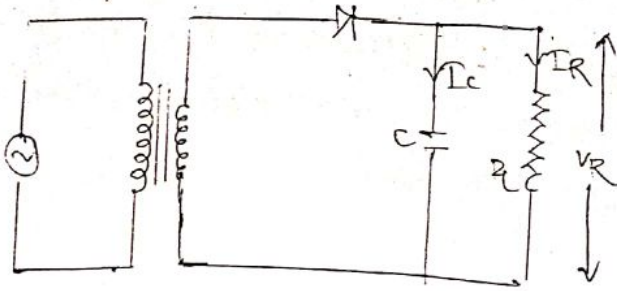

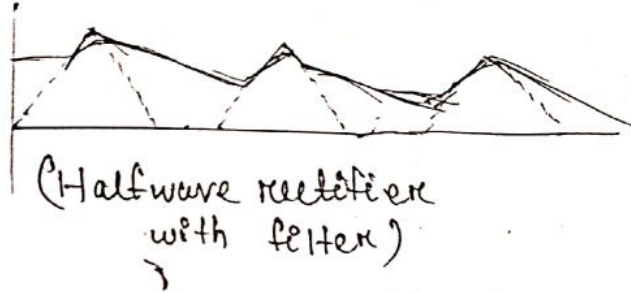
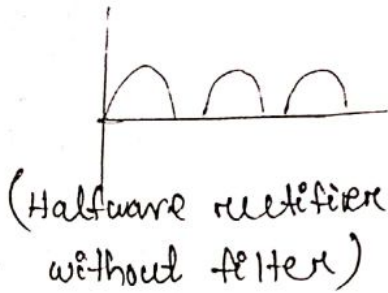
(Half wave rectifier with capacitor filter)




## choke

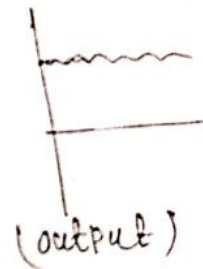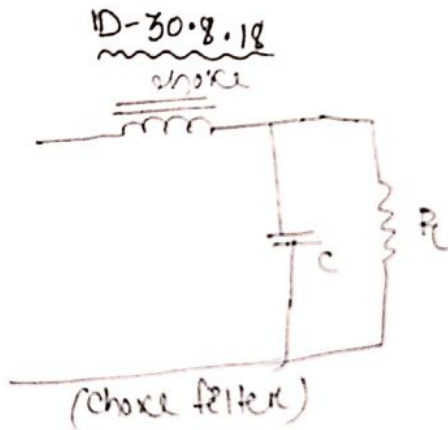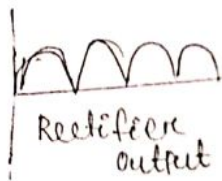

## π Filter

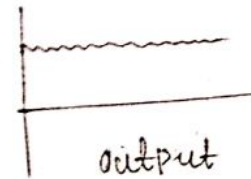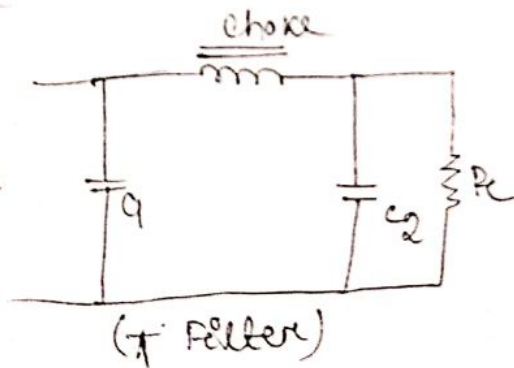

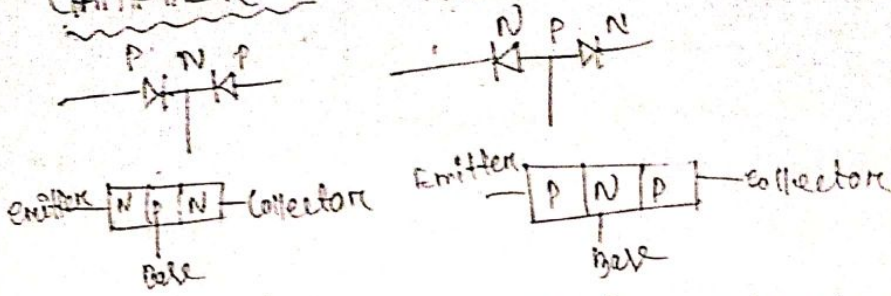



Emitter:- The emitter section is more heavily doped in comparison to other two region.

→ Emitter is always forward bias with respect to base.

Collector:- The collector is moderately doped.

→ The size of collector is more as compare to base as well as emitter.

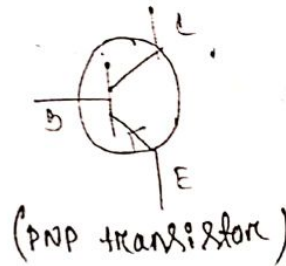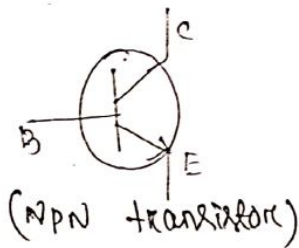
Base:- Base is lightly doped. Base is very thin as compare to either emitter or collector.




D-31.8.18

Transistor Biasing:-

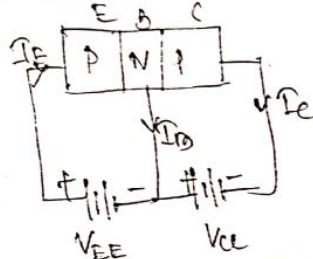The emitter base junction is always forward bias while the collector base junction is always reverse bias.



(PNP transistor biasing)

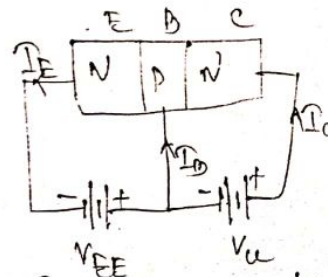


(NPN transistor biasing)

Different modes of operation of a transistor

There are 4 possible ways of biasing of a transistor these are called mode of operation of a transistor.

Cases	Base-emitter junction	Base-collector junction	mode of operation
1.	Forward bias	Reverse bias	Active
2.	Forward bias	forward bias	Saturation
3.	Reverse bias	Reverse bias	cutoff
4.	Reverse bias	Forward bias	Inverted

Current component in a transistor:

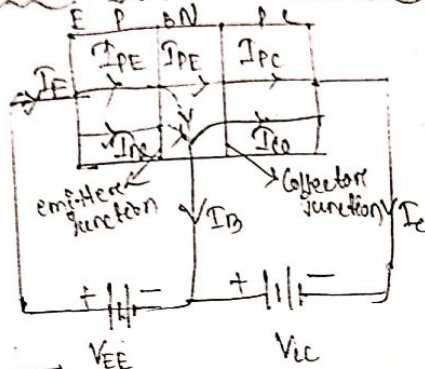

$$I_E = I_{PE} + I_{NE}$$

$$I_C = I_{PC} + I_{NC}$$

$$I_E = I_C + I_B$$

$I_{PE}$  = Hole current  $I_{PE}$  constituted by holes (holes crossing from emitter to base)

$I_{NE}$  = Electron current  $I_{NE}$  constituted by electrons.

Total emitter current  $I_E = I_{PE} + I_{NE}$

→ In commercial transistors the doping of emitter region is made much more heavier than base. & hence electron current component  $I_{NE}$  is negligible small in comparison with hole current  $I_{PE}$ .

→ The emitter current consists almost entirely of holes.


→ If the emitter were open circuited  $I_E = 0$  i.e.  $I_{PE} = 0$ . Under this condition the base and collector together act as a reverse diode and the collector current ( $I_{CO}$ ) = the reverse saturation current ( $I_{CS}$ ) which consists of following two parts:- (i)  $I_{CO}$  (ii)  $I_{PCO}$

(i)  $I_{CO}$  -  $I_{CO}$  caused by electron moving across  $Fe$  from p-region to n-region.

(ii)  $I_{PCO}$  -  $I_{CO}$  caused by hole moving across  $Fe$  from n-region to p-region.

$$I_{CO} = I_{PCO} + I_{CO}$$

act as an amplifier:-

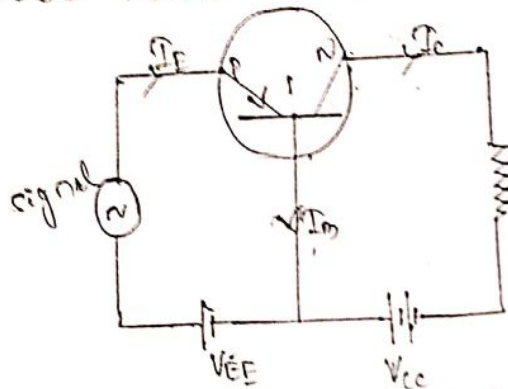

- The weak signal to be amplified is applied bet. emitter & base circuit & the output is taken across the load resistor  $R_L$  connected in the collector circuit.
- A dc voltage  $V_{EE}$  is also connected in the input circuit.
- A small change in signal voltage produce an appreciable change in emitter current because the input <sup>ext</sup> signal has low resistance.
- Due to transistor action the change in emitter current causes almost the change in collector current.
- When the collector current flow through the load resistor  $R_L$  a large voltage is developed across it.
- In this way the weak signal is applied in the input circuit appears in the amplified form across the output circuit. Thus the transistor act as an amplifier.

D-3.8.18



→ Thus the transistor act as an amplifier.

### Transistor circuit configuration:-



Transistor fit is of three types:-

- (i) Common base connection
- (ii) Common emitter connection
- (iii) Common collector connection


#### Common base:-

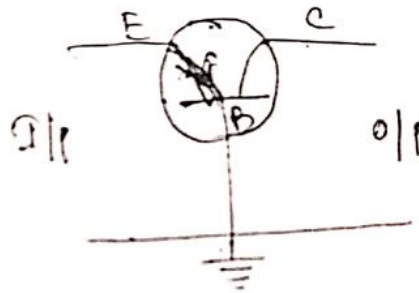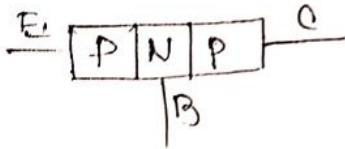

#### Common emitter:-

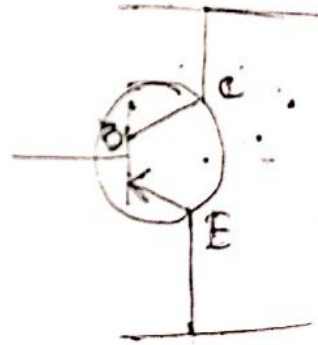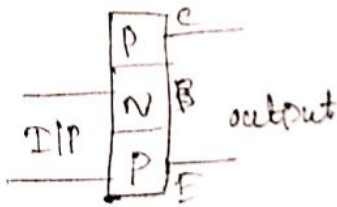

#### Common collector:-

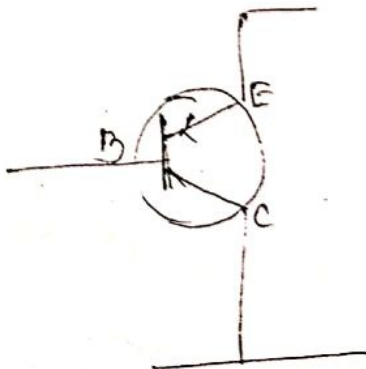



Transistor biasing:

Among the basic function of a transistor is its amplification. For faithful amplification being following three conditions must be satisfied.

- (i) The emitter base junction should be forward bias.
- (ii) Collector base junction should be reverse bias.
- (iii) There should be proper zero signal collector current, or proper operating point of a transistor.

Stabilisation:

The maintenance of operating point stable is known as

'Stabilisation'.

- There are two factors which are responsible for <sup>shifting the</sup> operating point.
- Many of the transistor parameters are markedly temp. sensitive and secondly when a transistor is replaced by another of the same time.
- So stabilisation of operating point is necessary due to following reason.

(i) Temperature dependence of  $I_c$ .

(ii) Individual variations

(iii) Thermal runaway

Temperature dependence of  $I_c$ :

- The collector <sup>leakage</sup> current  $I_{c0}$  is greatly influence by temp. change.

- Increase in  $\beta$  with increase in temp.

- The instability of  $I_c$  is caused by above two reason.

Individual variations:

- When a transistor is replaced by another transistor of same time the value of  $\beta$  &  $V_{BE}$  are not exactly same.
- Hence the operating point is change.

## Thermal runaway:-

- If the temp. increases beyond particular range then transistor burned out.
- The range of temp. lies bet<sup>n</sup> 60° to 100°c for germanium transistor and 150°- 225°c for silicon.
- The increase in collector junction temp is due to thermal runaway.
- When a collector current flow in a transistor it is heated. its temp. increases.
- If no stabilisation is done the collector leakage current also increases.
- This further increases transistor temperature.
- The action become cumulative for the transistor. may ultimately burnout.
- This self destruction of an unstabilised transistor is known as 'thermal runout'.

## Stability Factor:-

- The stability factor (S) is defined as the rate of change of collector current  $I_c$  w.r.t reverse saturation current  $I_{co}$ . keeping  $\beta$  &  $V_{BE}$  constant.

$$S = \frac{\partial I_c}{\partial I_{co}} = \frac{\Delta I_c}{\Delta I_{co}}$$

## Expression for stability factor (S):-

- when a transistor is biased in active region of its characteristics the collector current  $I_c$  is related to base current ( $I_b$ ) by following expression.

$$I_c = \beta I_b + (1 + \beta) I_{co}$$

- differentiating eq<sup>n</sup> w.r.t  $I_c$ . considering  $\beta$  to be const. we get

we get,  $\frac{dI_B}{dI_C} = \frac{dI_{B0}}{dI_C} + \frac{d(C+P)I_{C0}}{dI_C}$

$$\Rightarrow 1 = \beta \frac{dI_B}{dI_C} + (1+\beta) \frac{dI_{C0}}{dI_C}$$

$$\Rightarrow 1 = \beta \frac{dI_B}{dI_C} + (1+\beta) \frac{1}{S}$$

$$\Rightarrow 1 - \beta \frac{dI_B}{dI_C} = (1+\beta) \frac{1}{S}$$

$$\Rightarrow \frac{1}{S} (1+\beta) = 1 - \beta \frac{dI_B}{dI_C}$$

$$\Rightarrow \frac{1+\beta}{1 - \beta \frac{dI_B}{dI_C}} = S$$

$$\Rightarrow S = \frac{1+\beta}{1 - \beta \frac{dI_B}{dI_C}}$$

10-6.9.18

### Different method of transistor biasing:-

Some of the method used for providing bias for transistor are as follows:-


(i) Base resistor method

(ii) Collector to base bias

(iii) base bias with collector & emitter feedback.

(iv) voltage divider bias

### Base resistor method:-

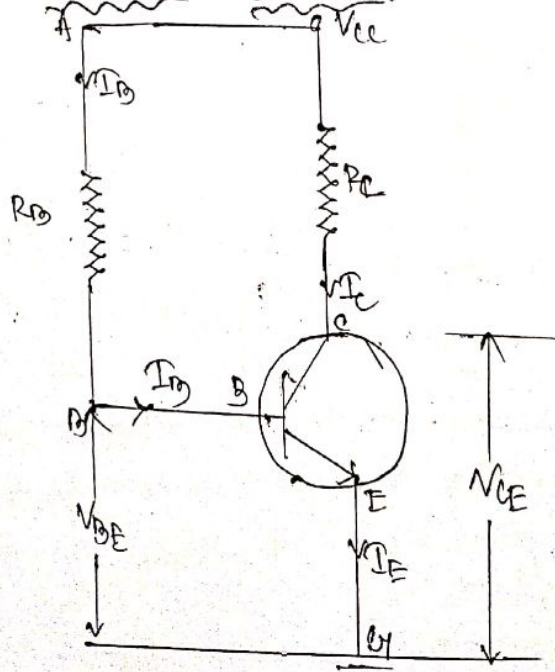

(CE NPN transistor with base resistor method)

- In this method a high resistance  $R_B$  is connected between the terminal of supply  $V_{CC}$  and base of the transistor.
- The required zero signal base current flows through  $R_B$  and is provided by  $V_{CC}$ .
- The base emitter junction is forward biased because the base is positive w.r.t emitter.

### Analysis

Considering the closed circuit ABEDCA and apply KVL:

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$\Rightarrow I_B R_B = V_{BE} - V_{CC}$$

$$\Rightarrow I_B R_B = V_{CC} - V_{BE}$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

Further  $\beta = \frac{I_C}{I_B}$

$$\Rightarrow I_C = \beta I_B$$

$$\Rightarrow I_B = \frac{I_C}{\beta}$$

Putting the value of  $I_B = \frac{I_C}{\beta}$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\Rightarrow \frac{I_C}{\beta} = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\Rightarrow I_C = \frac{(V_{CC} - V_{BE}) \beta}{R_B}$$

The value of  $V_{BE}$  can be seen from transistor manual.  
The value of  $R_B$  can be calculated as  $V_{BE}$  is generally very small as compared to  $V_{CC}$  hence

$$I_C = \frac{V_{CC} \beta}{R_B}$$

$$R_B = \frac{V_{CC} \beta}{I_C}$$

The value of  $\beta$  can found directly. Hence this method is some time called as time bias method.

Stability factor (S): -

$$S = \frac{1 + \beta}{1 - \beta \left( \frac{d\beta}{dI_C} \right)}$$

$$S = \frac{1 + \beta}{1 - \beta(0)} \quad (\because \beta \text{ is independent } \frac{d\beta}{dI_C} = 0)$$

$$S = 1 + \beta$$

if  $\beta = 100$  then  $S = 101$ , this shows  $I_C$  change 101 times as much as any change in  $I_{C0}$ .

$I_C$  is very dependent upon  $I_{C0}$ . Hence upon temperature.


The value of S is the heights that can obtained.

Hence the circuit has very poor stability.

D-7.8.18

Collector to base bias:

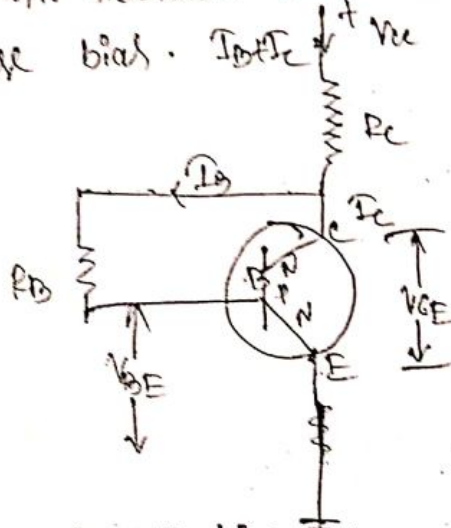The ext of an NPN transistor connected in C configuration with collector to base bias.



- The ext is same as base bias ext except that the base resistor  $R_B$  is returned to collector greater than to  $V_{CC}$  supply.
- using this ext there is considerable improvement in the stability.
- If the collector current  $I_C$  tends to increase consequently  $V_{CE}$  decreases as a result base current  $I_{BE}$  also decrease.
- This will tend to compensate for the original increase.

Analysis

voltage drop across  $R_e = (I_B + I_E)R_e$ , apply KVL to input loop

$$V_{CC} - I_E R_e - I_B R_B - V_{BE} = 0$$

$$\Rightarrow V_{CC} = I_E R_e + I_B R_B + V_{BE}$$

$$\Rightarrow I_B R_B = V_{CC} - I_E R_e - V_{BE}$$

$$\Rightarrow R_B = \frac{V_{CC} - I_E R_e - V_{BE}}{I_B}$$

$$\text{we know } \beta = \frac{I_E}{I_B}$$

$$\Rightarrow I_B = \frac{I_E}{\beta}$$

Put in eq<sup>n</sup>

$$R_B = \frac{(V_{CC} - I_E R_e - V_{BE})\beta}{I_E}$$

Stability Factor (S):-

$$V_{CC} - (I_B + I_E)R_e - I_B R_B - V_{BE} = 0$$

$$\Rightarrow V_{CC} - I_B R_e - I_E R_e - I_B R_B - V_{BE} = 0$$

$$\Rightarrow V_{CC} - I_B (R_e + R_B) - I_E R_e - V_{BE} = 0$$

$$\Rightarrow I_B (R_e + R_B) = V_{CC} - I_E R_e - V_{BE}$$

$$\Rightarrow I_B = \frac{V_{CC} - I_E R_e - V_{BE}}{R_e + R_B}$$

since  $V_{BE}$  is almost independent of collector current ( $I_C$ )

( $V_{BE} = 0.7$  for silicon,  $0.3$  for Ge)

$$I_B = \frac{V_{CC}}{R_e + R_B} - \frac{I_E R_e}{R_e + R_B} - \frac{V_{BE}}{R_e + R_B}$$

$$\Rightarrow \frac{dI_B}{dI_E} = \frac{-R_e}{R_e + R_B} \cdot \frac{dI_E}{dI_E} \quad \left( \because \frac{V_{CC}}{R_e + R_B} \text{ and } \frac{V_{BE}}{R_e + R_B} \text{ is const} = 0 \right)$$

$$\Rightarrow \frac{dI_B}{dI_E} = \frac{-R_e}{R_e + R_B} \cdot 1$$

$$\Rightarrow \frac{dI_B}{dI_E} = \frac{-R_e}{R_e + R_B}$$


$$S = \frac{1+\beta}{1-\beta \left( \frac{dI_E}{dI_C} \right)} = \frac{1+\beta}{1-\beta \left( \frac{-R_E}{R_E + R_B} \right)}$$

$$= \frac{1+\beta}{1+\beta \left( \frac{R_E}{R_E + R_B} \right)}$$

↳ This value is smaller than  $1+\beta$  which is obtained for base resistor method. Thus there is an improvement in stability.

Self bias or emitter bias (voltage divider bias)

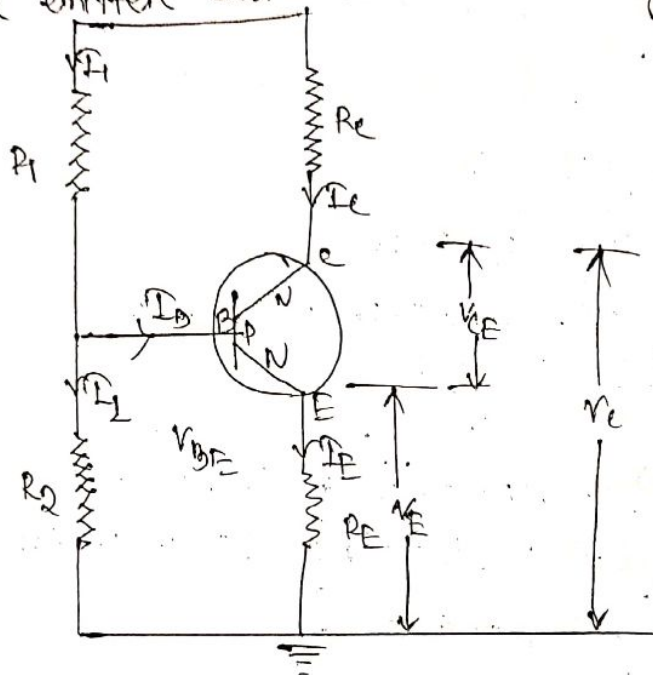↳ A very small commonly used biasing arrangement is self bias or emitter bias. The circuit arrangement is shown.



↳ This is known as universal bias stabilization ext. In this method two resistance  $R_1$  &  $R_2$  connected across supply voltage  $V_{CC}$  provide biasing.

↳ The emitter resistance  $R_E$  provide stabilisation the name voltage divider is derived due to fact their resistors  $R_1$  &  $R_2$  form a potential divider across  $V_{CC}$ .

↳ The resistance  $R_E$  causes a voltage drop in a direction as to reverse bias reduce the increase in  $I_E$  and improves the operating point stability.

### ANALYSIS:-

Let current  $I_1$  flows through  $R_1$  as base current. Its very small the current flowing through  $R_2$  can also be taken as  $I_1$ , the calculation of collector current.

The current  $I_1$  flowing through  $R_1$  &  $R_2$  is given by

$$I_1 = \frac{V_{CC}}{R_1 + R_2}$$

The voltage  $V_2$  developed across  $R_2$  is given by

$$V_2 = \left( \frac{R_2}{R_1 + R_2} \right) \times V_{CC}$$

Applying KVL to the base circuit

$$V_2 = V_{BE} + I_E R_E$$

$$\Rightarrow V_2 = V_{BE} + I_E R_E$$

$$\Rightarrow V_2 = V_{BE} + I_E R_E \quad (\because I_E = I_C)$$

∴

$$I_E = \frac{V_2 - V_{BE}}{R_E}$$

Here  $I_E$  almost independent of transistor parameter. Hence good stabilizing is ensured.

Applying KVL to output side

$$V_{CC} - I_C R_C - I_E R_E - V_{CE} = 0$$

$$\Rightarrow V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$\Rightarrow V_{CE} = V_{CC} - I_C R_C - I_E R_E \quad (\because I_C \approx I_E)$$



$$\Rightarrow V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$\Rightarrow V_{CE} = V_{CC} - I_C (R_C + R_E)$$




Circuit analysis using Thevenin's theorem:

current  
can also  
+  
given by  
by

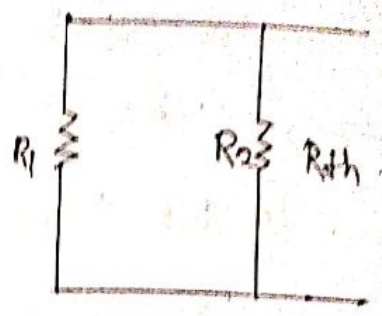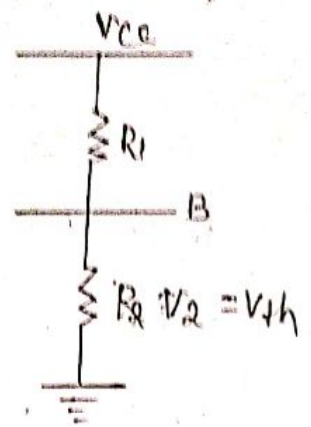

$$V_2 = V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC}$$
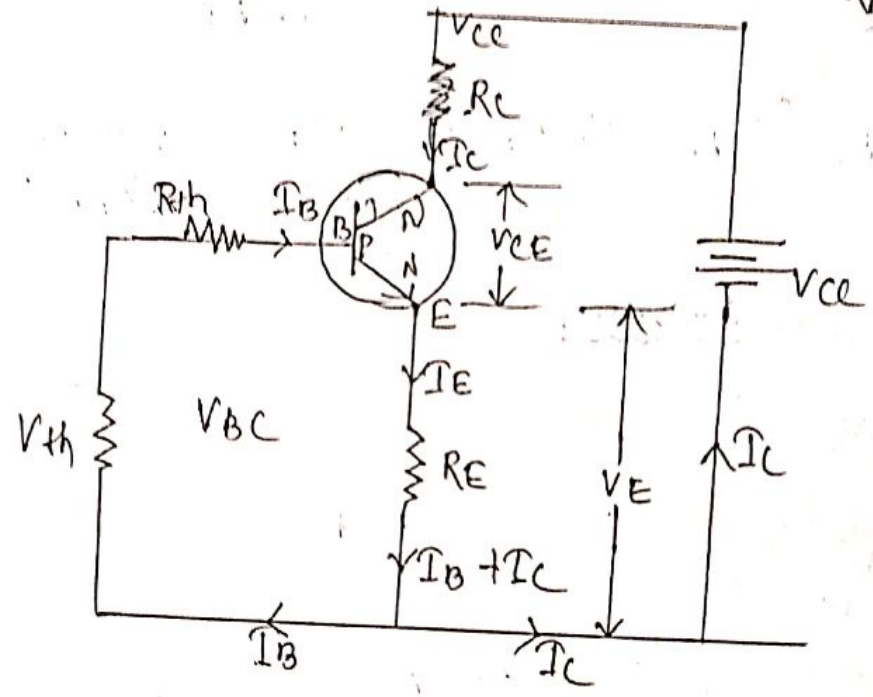
$$R_{th} = R_1 \parallel R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2}$$



(Simplified equivalent circuit)

Applying KVL to base-emitter circuit

$$V_{th} - I_B R_{th} - V_{BE} - (I_B + I_C) R_E = 0$$

$$V_{th} = I_B R_{th} + V_{BE} + (I_B + I_C) R_E$$

Applying KVL to emitter-collector circuit.

$$V_{CC} - V_{CE} + I_C (R_E - R_C) = 0 \quad (\because I_C \gg I_B)$$

$$\Rightarrow I_C (R_C + R_E) = V_{CC} - V_{CE}$$

$$\Rightarrow I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E}$$

Substituting the value of  $I_C$  in  $V_{th}$  eq<sup>n</sup>.

$$V_{th} = I_B R_{th} + V_{BE} + (I_B + I_C) R_E$$

$$\Rightarrow V_{th} = I_B R_{th} + V_{BE} + \left( I_B + \frac{V_{CC} - V_{CE}}{R_C + R_E} \right) \cdot R_E$$

$$\Rightarrow V_{th} = I_B R_{th} + V_{BE} + I_B R_E + \frac{V_{CC} - V_{CE}}{R_C + R_E} \times R_E$$

$$\Rightarrow V_{th} = I_B R_{th} + V_{BE} + I_B R_E + \frac{V_{CC} \times R_E}{R_C + R_E} - \frac{V_{CE} \times R_E}{R_C + R_E}$$

10-8.9.18

Stability Factor:-

$$V_{th} = I_B R_{th} + V_{BE} + I_B R_E$$

Considering  $R_{th} = R_B$

$$V_{th} = I_B R_B + V_{BE} + (I_B + I_C) R_E$$

differentiate eq<sup>n</sup> with respect to  $I_C$

$$\Rightarrow 0 = \frac{dI_B}{dI_C} R_B + 0 + \left( \frac{dI_B}{dI_C} + 1 \right) R_E$$

$$\Rightarrow \frac{dI_B}{dI_C} R_B + \frac{dI_B}{dI_C} R_E + R_E = 0$$

$$\Rightarrow \left( \frac{dI_B}{dI_C} \right) \{ R_B + R_E \} + R_E = 0$$

$$\Rightarrow \frac{dI_B}{dI_C} \cdot (R_B + R_E) = -R_E$$

$$\Rightarrow \frac{dI_B}{dI_C} = \frac{-R_E}{R_B + R_E}$$

we know that, the stability factor is given by

$$S = \frac{1+\beta}{1-\beta \left( \frac{dI_B}{dI_C} \right)}$$

$$S = \frac{1+\beta}{1-\beta \left( \frac{-R_E}{R_B+R_E} \right)}$$

$$S = \frac{1+\beta}{1+\beta \left( \frac{R_E}{R_B+R_E} \right)}$$

we can also written as

$$S = \frac{1+\beta}{1+\beta \left( \frac{1}{\frac{R_B}{R_E} + 1} \right)}$$

$$\Rightarrow S = \frac{1+\beta}{1 + \beta \frac{R_E}{R_B + R_E}}$$

$$\Rightarrow S = \frac{(1+\beta)(R_B+R_E)}{R_B+R_E+\beta R_E}$$

$$\Rightarrow S = \frac{(1+\beta) \left( \frac{R_B}{R_E} + 1 \right)}{\frac{R_B}{R_E} + 1 + \beta} \quad (\because \text{divided } R_E)$$

$$\Rightarrow S \left( \frac{R_B}{R_E} \right) + S + S\beta = (1+\beta) \left( \frac{R_B}{R_E} + 1 \right)$$

$$\Rightarrow S \left( \frac{R_B}{R_E} \right) + S + S\beta = 1 + \beta + \frac{R_B}{R_E} + \beta \frac{R_B}{R_E}$$

$$\Rightarrow -1 - \beta + S + S\beta = \frac{R_B}{R_E} + \beta \frac{R_B}{R_E} - S \frac{R_B}{R_E}$$

$$\Rightarrow \beta(S-1) + (S-1) = \frac{R_B}{R_E} \cdot (1+\beta - S)$$

$$\Rightarrow (S-1)(1+\beta) = \frac{R_B}{R_E} (1+\beta - S)$$

$$\Rightarrow \frac{R_B}{R_E} = \frac{(S-1)(1+\beta)}{1+\beta - S}$$

Q:- A silicon transistor w/ potential divider method

of biasing,  $V_{CC} = 12\text{V}$ ,  $R_1 = 10\text{k}\Omega$ ,  $R_2 = 5\text{k}\Omega$ ,  $R_L = 1\text{k}\Omega$ ,  
 $R_E = 3\text{k}\Omega$  determine operating point <sup>using</sup> thevenin's theorem.

$$V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC}$$
$$= \frac{5}{10+5} \times 12$$
$$= 4\text{V}$$

$$R_{th} = R_1 \parallel R_2$$
$$= \frac{R_1 \times R_2}{R_1 + R_2} = \frac{10 \times 5}{10+5} = 3.33\text{k}\Omega$$

$$V_{th} = I_B R_{th} + V_{BE} + (I_B + I_C) R_E$$

$$\Rightarrow V_{th} = I_B R_{th} + V_{BE} + I_C R_E \quad (\because I_C \gg I_B)$$

$$\Rightarrow V_{th} = I_B R_{th} + V_{BE} + \beta I_B R_E$$

$$\Rightarrow V_{th} - V_{BE} = I_B (R_{th} + \beta R_E)$$

$$\Rightarrow I_B = \frac{V_{th} - V_{BE}}{R_{th} + \beta R_E}$$

$$\Rightarrow \frac{I_C}{\beta} = \frac{V_{th} - V_{BE}}{R_{th} + \beta R_E} \quad (\because I_C = \beta I_B \Rightarrow I_B = \frac{I_C}{\beta})$$

$$\Rightarrow \frac{I_C}{\beta} = \frac{V_{th} - V_{BE}}{\beta \left( \frac{R_{th}}{\beta} + R_E \right)}$$

$$\Rightarrow I_C = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta} + R_E}$$

$$\Rightarrow I_C = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{\beta} + R_E} \quad (\because \frac{R_{th}}{\beta} \ll R_E)$$

$$\Rightarrow I_C = \frac{V_{th} - V_{BE}}{R_E}$$

$$= \frac{4 - 0.7}{3} = \frac{3.3}{3} = 1.1\text{mA}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$\Rightarrow V_{CE} = 12 - 1.1(1+3)$$

$$\Rightarrow V_{CE} = 12 - 1.1(4) \\ = 7.6 \text{ volt}$$

Operating point (7.6V, 1.1mA)

$$\underline{D - 10.9 \cdot 18}$$

Q<sub>2</sub> - A germanium transistor is to be operated at zero signal  $I_C = 1 \text{ mA}$ . If the collector supply  $V_{CC} = 10 \text{ V}$ , what is the value of  $R_B$  in base resistor method (i) take  $\beta = 100$ .  
 (ii) If another transistor of same batch with  $\beta = 50$  what will be the value of  $I_C$  zero signal  $I_C$  for same  $R_B$ .

$$I_C = 1 \text{ mA}$$

$$V_{CC} = 10 \text{ V}$$

$$(i) R_B = \frac{(V_{CC} - V_{BE}) \beta}{I_C}$$

$$= \frac{10 - 0.3 \text{ V} \times 100}{1 \text{ mA}}$$

$$= 970000$$

$$= 970 \text{ k}\Omega$$

$$(ii) \beta = 50$$

$$I_C = \frac{(V_{CC} - V_{BE}) \beta}{R_B}$$

$$= \frac{(10 - 0.3) 50}{970 \times 10^3}$$

$$= \frac{9.7 \times 50}{970 \times 10^3} = 5 \times 10^{-4} \text{ A}$$

$$= 0.5 \text{ mA}$$

Q. A silicon transistor with  $\beta = 100$  and biased by base resistor method determine operating point.

$$I_B = \frac{(V_{CC} - V_{BE}) \beta}{R_B}$$

$$= \frac{(10 - 0.7) 100}{930 \times 10^3}$$

$$= 1 \times 10^{-3}$$


$$= 1 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 10 - 1 \times 10^{-3} \times 4 \times 10^3$$

$$= 10 - 4$$

$$= 6 \text{ V}$$

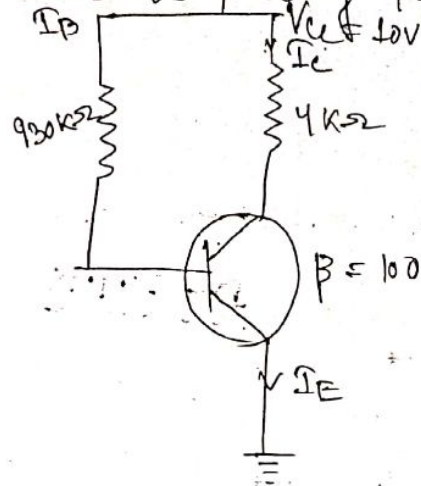

operating point  $V_{CE} = 6 \text{ V}$ ,  $I_C = 1 \text{ mA}$

operating point  $(6 \text{ V}, 1 \text{ mA})$

Q. It is required to set operating point by biasing with feedback resistor at  $I_C = 1 \text{ mA}$ ,  $V_{CE} = 6 \text{ V}$  if  $\beta = 100$ ,  $V_{CC} = 10 \text{ V}$ ,  $V_{BE} = 0.3 \text{ V}$  How will you do it.

(1) What will be the new operating point if  $\beta = 50$  and all other circuit value will remain same.

$$R_C = \frac{V_{CC} - V_{CE}}{I_C}$$

$$= \frac{10 - 6 \text{ V}}{1 \text{ mA}} = \frac{4 \text{ V}}{1 \text{ mA}} = 4 \text{ k}\Omega$$

$$R_B = \frac{(V_{CC} - V_{BE}) - I_C R_C}{I_B} \beta$$

$$= \frac{(10 - 0.3 - 1 \times 10^{-3} \times 4 \times 10^3) 100}{1 \times 10^{-3}}$$

$$= 570 \text{ k}\Omega$$

$$= 570 \text{ k}\Omega$$

$$I_c = \frac{V_{cc} - V_{CE}}{R_c}$$

$$= \frac{10 - 6}{4 \times 10^3}$$

(11)  $\beta = 50$

$$R_B = \frac{(V_{cc} - V_{BE} - I_c R_c) \beta}{I_c}$$

$$\Rightarrow 540 \times 10^3 = \frac{(10 - 0.7 - I_c \times 4 \times 10^3) 50}{I_c}$$

$$\Rightarrow 540 \times 10^3 \times I_c = 9.7 \times 50 - I_c \times 4 \times 10^3 \times 50$$

$$\Rightarrow I_c (540 \times 10^3 + 200 \times 10^3) = 9.7 \times 50$$

$$\Rightarrow I_c = \frac{9.7 \times 50}{540 \times 10^3 + 200 \times 10^3}$$

$$= \frac{9.7 \times 50}{740 \times 10^3} = \frac{9.7 \times 50}{740 \times 10^3}$$

$$= 0.63 \text{ mA}$$

$$V_{CE} \leq V_{cc} - V_{CE} - I_c R_c \rightarrow 0$$

$$\Rightarrow V_{CE} = V_{cc} - I_c R_c$$

$$= 10 - 0.63 \times 10^{-3} \times 4 \times 10^3$$

$$= 10 - 0.63 \times 4$$


$$= 7.48 \text{ V}$$

New operating point  $(V_{CE}, I_c) = (7.48 \text{ V}, 0.63 \text{ mA})$

D-11-9-14 TRANSISTOR AMPLIFIER Chapter

- ⇒ One of the most important function of electronic ext is amplification.
- ⇒ In absence of this property many other specific circuit function could not be possible.
- ⇒ For example oscillator to produce sine wave, square wave or any other desired wave shape could not be possible.
- Almost all electronic system use amplifier.
- \* so an amplifier is defined as a devices that increases the voltage, current or power of an input signal with aid of transistor.

Practical ckt of transistor amplifier:-

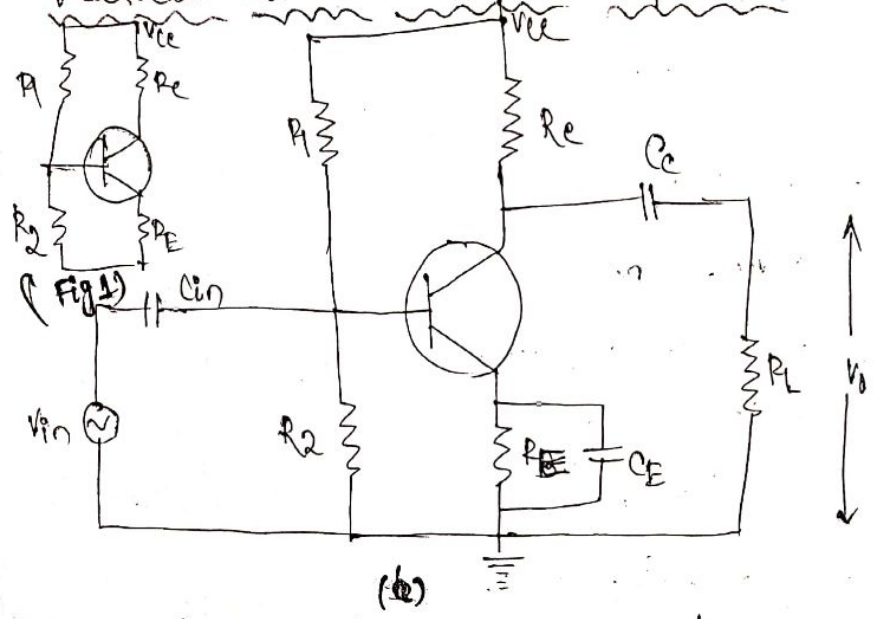

- ⇒ A practical ckt of transistor amplifier in common emitter configuration is shown in above figure.
- ⇒ Fig (a) represent the voltage divider biasing circuit.
- The various ckt elements and their function are :-



$R_1, R_2, R_E$  from the biasing and stabilization circuit.

Load  $R_L$ :-

The resistance  $R_L$  is connected across the output is known as load. When a number of stages is used then,  $R_L$  represents the input resistance of next stage.

Coupling capacitance  $C_C$ :-

- The capacitor passes ac signal from one side to another. Its value is approximately 10 $\mu$ F.
- This is also known as 'blocking capacitance' because it does not allow the dc voltage to pass through it.
- Due to presence of  $C_C$  the output across the resistor  $R_L$  is free from the collector dc voltage.

(iv) Input capacitor  $C_{in}$ :-

- This capacitor couples the signal to the base of transistor.
- This is an electrolyte capacitor of value of approximately 100 $\mu$ F.
- In absence of this capacitor, the source resistance will come in parallel with  $R_2$  and thus change the bias.


(v) Emitter bypass capacitor  $C_E$ :-

- This capacitor  $C_E$  acts as a bypass capacitor. Its value is approximately 100 $\mu$ F.
- This provides a low reactance path to amplified ac signal.
- In presence of  $C_E$  amplified ac signal will pass through this.
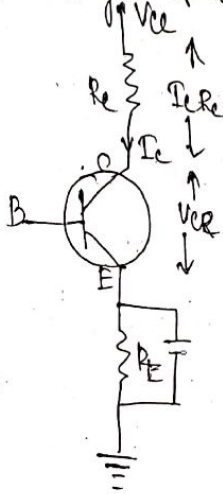
### DC load line:-

The DC load line is a line on the output characteristics of a transistor which gives the value of  $I_c$  and  $V_{ce}$  corresponding to zero signal condition.

Consider the ~~op~~ voltage of base amplifier ~~cut~~:-



Consider the o/p. voltage of the base amplifier ~~cut~~ shown in fig.;

Applying KVL we have,

$$V_{cc} - I_c R_c - V_{ce} - I_e R_e = 0$$

$$\Rightarrow V_{ce} = V_{cc} - I_c R_c - I_e R_e$$

$$\Rightarrow \boxed{V_{ce} = V_{cc} - I_c (R_c + R_e)} \quad (\because I_c \approx I_e)$$

Hence  $V_{cc}$  &  $R_c + R_e$  is constant, therefore it represents a straight line known as Load line.

The load line can be plotted in following way:-


(i) when we put  $I_c = 0$  the  $V_{ce}$  would be  $\text{max}^m$

$$V_{ce} (\text{max}) = V_{cc}$$

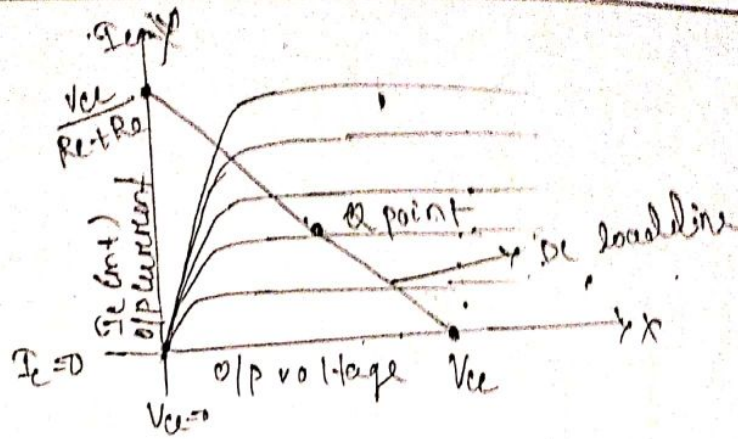(ii) when we put  $V_{ce} = 0$  then;


$$0 = V_{cc} - I_c (R_c + R_e)$$

$$\Rightarrow \boxed{I_c = \frac{V_{cc}}{R_c + R_e}}$$



DC equivalent ckt :-

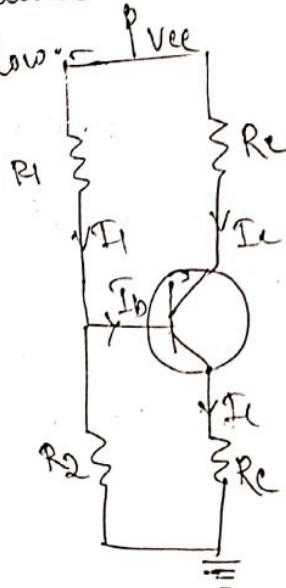In case of DC equivalent ckt no signal is applied and all the capacitors look like open ckt. Thus to draw the equivalent ckt we open all the capacitors and reduce all ac sig source to zero.  
 The DC equivalent ckt of a transistor amplifier is shown below:-




(DC equivalent ckt)

D-18.9.18

AC equivalent circuit:-

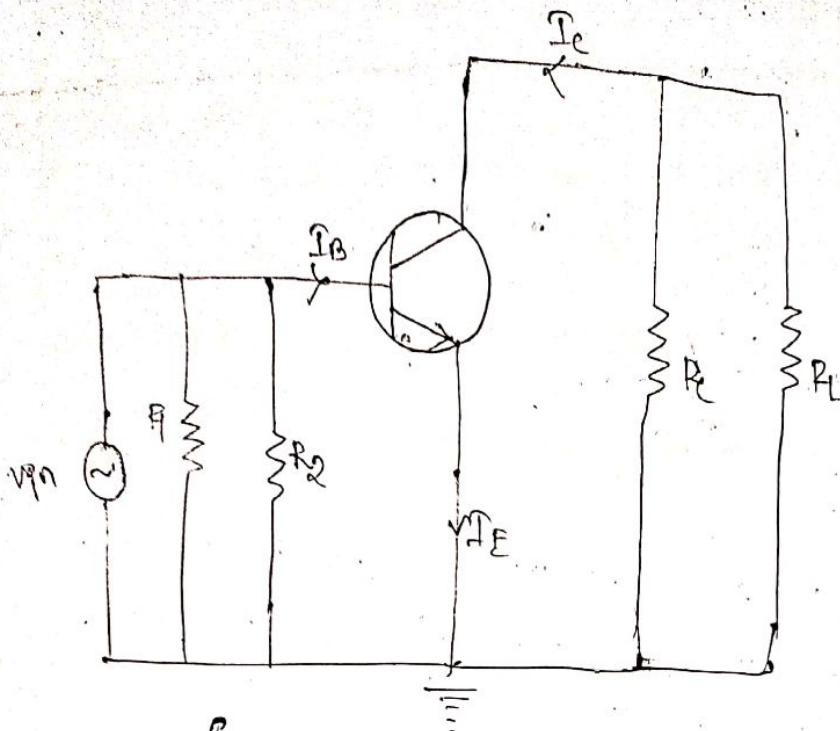- ⇒ For AC equivalent ckt only ac conditions are to be considered.
- ⇒ In this case the variations are so fast that the capacitor may be treated as short ckt.
- ⇒ We need not consider DC supply.
- ⇒ In order to draw AC equivalent ckt we replace all DC sources to zero & a short ckt all the capacitors.



(AC equivalent circuit)

### AC load line

⇒ The variation in the collector current & voltage are seen with the help of ac load line. Corresponding to this ac load. Hence ac load line is different from dc load line.

⇒ As regards ac signals the transistor amplifier ac load  $R_{ac}$ .


$$R_{ac} = R_C \parallel R_L$$

$$R_{ac} = \frac{R_C \cdot R_L}{R_C + R_L}$$

⇒ Max<sup>m</sup> collector-emitter voltage =  $V_{CE} + I_C R_{ac}$ .

This locate a point on collector-emitter voltage axis.

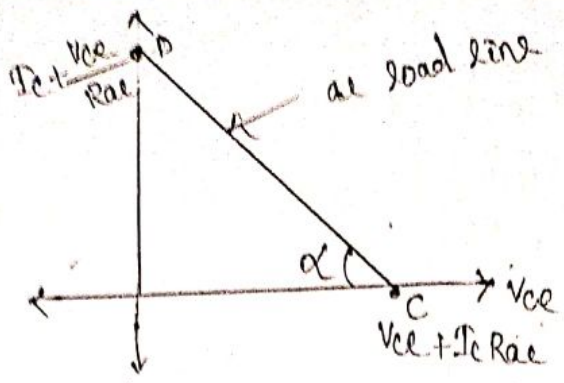⇒ Max<sup>m</sup> collector current =  $I_C + \frac{V_{CE}}{R_{ac}}$ . This locate a point on collector current axis.



slope of ac load line:-

The slope of load line is given by;  $\tan \alpha =$

$$\begin{aligned} \tan \alpha &= \frac{OD}{OC} \\ &= \frac{I_c + \frac{V_{ce}}{R_{ac}}}{V_{ce} + I_c R_{ac}} \\ &= \frac{I_c + \frac{V_{ce}}{R_{ac}}}{R_{ac} \left( I_c + \frac{V_{ce}}{R_{ac}} \right)} \end{aligned}$$

$$\begin{aligned} &= \frac{I_c + \frac{V_{ce}}{R_{ac}}}{V_{ce} + I_c R_{ac}} \\ &= \frac{I_c R_{ac} + V_{ce}}{R_{ac} (V_{ce} + I_c R_{ac})} = \frac{1}{R_{ac}} \end{aligned}$$

$$\text{Slope} = \frac{1}{R_{ac}}$$

Calculation of Gain:-

Current gain =  $\frac{I_c(\text{max}) - I_c(\text{min})}{I_b(\text{max}) - I_b(\text{min})}$

Voltage gain =  $\frac{V_{ce}(\text{max}) - V_{ce}(\text{min})}{V_{in}(\text{max}) - V_{in}(\text{min})}$

ID-22.9.18

Calculation of gain using cut analysis:-

$$\begin{aligned} R_{ac} &= R_e \parallel R_L \\ &= \frac{R_e \cdot R_L}{R_e + R_L} \end{aligned}$$

$$R_{in} = R_1 \parallel R_2$$

voltage gain =  $\frac{V_{out}}{V_{in}}$

output voltage =  $I_c \times R_{ac}$

$$\text{Input voltage} = I_b \times R_{in}$$

$$\text{voltage gain} = A_v = \frac{V_{out}}{V_{in}}$$

$$= \frac{I_c \times R_{ac}}{I_b \times R_{in}}$$

$$= \frac{I_c}{I_b} \times \frac{R_{ac}}{R_{in}}$$

$$= \beta \times \frac{R_{ac}}{R_{in}} \quad \left( \because \frac{I_c}{I_b} = \beta \right)$$

$$\text{Power gain} = A_p = \frac{\text{Output power}}{\text{Input power}}$$

$$= \frac{I_c^2 \times R_{ac}}{I_b^2 \times R_{in}}$$

$$= \frac{I_c^2}{I_b^2} \times \frac{R_{ac}}{R_{in}}$$

$$A_p = \beta^2 \times \frac{R_{ac}}{R_{in}} \quad \left( \because \frac{I_c^2}{I_b^2} = \beta^2 \right)$$

Q.1  $R_e = 5k\Omega$ ,  $R_L = 10k\Omega$ ,  $\beta = 100$ ,  $R_{in} = 2k\Omega$ , find the ac load  $R_{ac}$

voltage gain & power gain.

$$R_{ac} = \frac{5 \times 10}{5 + 10} = 3.33$$

$$A_v = \beta \times \frac{3.33}{2} = 166.5$$





$$A_p = (100)^2 \times \frac{3.33}{2} = 16650$$

1
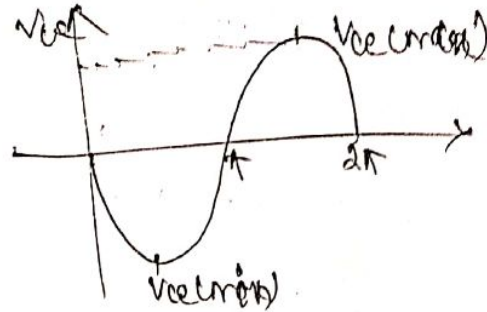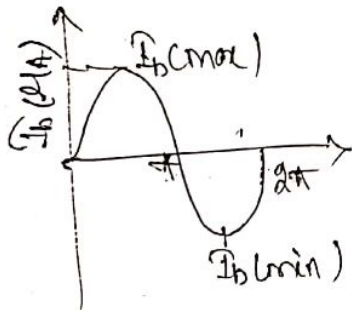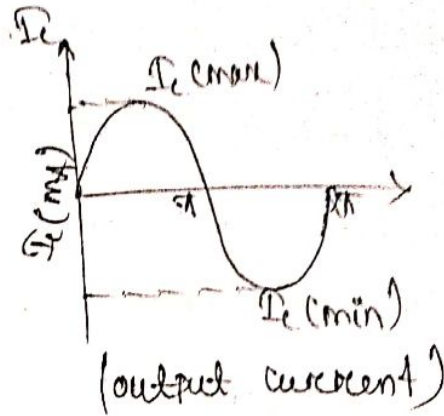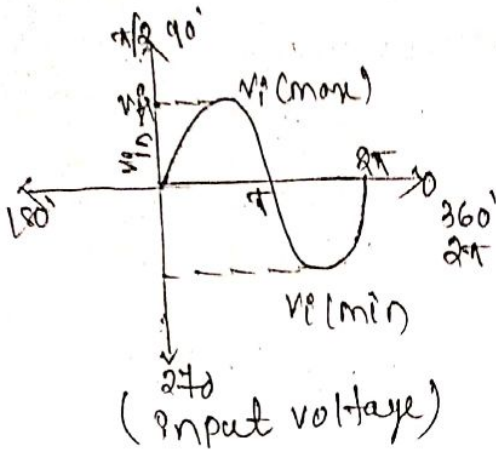
## Phase Reversals

36

The phase difference of  $180^\circ$  bet<sup>n</sup> i/p voltage & o/p voltage in common emitter amplifier is known as "Phase reversal".



(Input current)

(Collector emitter voltage)

When the base current is max<sup>m</sup> in -ve direction  
Collector emitter voltage ( $V_{CE}$ ) is max<sup>m</sup> in +ve direction.  
In this way the i/p and the o/p voltage are in  
opposite phase. Thus the transistor produce  $180^\circ$   
Phase reversal bet<sup>n</sup> i/p & o/p voltage.

D-27.8.18

CHAPTER D-5.11.18 HYBRID MODEL

Hybrid Model (H-parameter) -

$$V_1, i_2 = f(i_1, V_2)$$

Here,  $V_1, i_2$  are two dependent parameter.

$i_1, V_2$  are two independent parameter.

we have to represent  $V_1$  in terms of parameter  $i_1$  &  $V_2$ .

Similarly,

we represent  $i_2$  in terms of parameter  $i_1$  &  $V_2$ .

$$V_1 = h_{11} i_1 + h_{12} V_2$$

$$i_2 = h_{21} i_1 + h_{22} V_2$$

Assuming short circuit condition in o/p port  
 $V_2 = 0$


$$V_1 = h_{11} i_1 \quad (h_{11} = \frac{V_1}{i_1} \text{ (input impedance)})$$

$$i_2 = h_{21} i_1 \quad (h_{21} = \frac{i_2}{i_1} \text{ (Forward current gain)})$$

Assuming open circuit condition in i/p port  
 $i_1 = 0$

$$V_1 = h_{12} V_2 \quad (h_{12} = \frac{V_1}{V_2} \text{ reverse voltage gain})$$
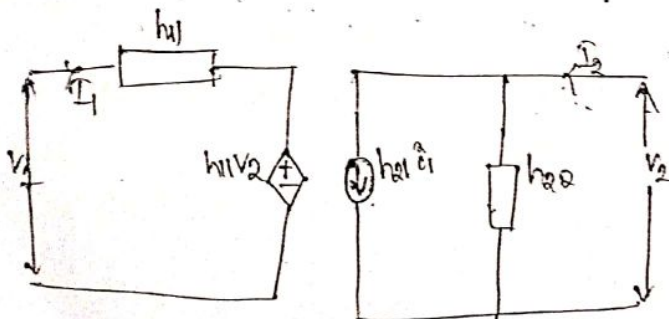
$$i_2 = h_{22} V_2 \quad (h_{22} = \frac{i_2}{V_2} \text{ output admittance})$$





Simp  
Simplified CE hybrid parameters-

We use hybrid parameters  $h_{11}, h_{12}, h_{21}, h_{22}$  in different transistor configuration such as:- Common base, Common collector, Common emitter.

- \* For Common emitter,
  - $h_{11}$  = input impedance.
  - we use this parameter as:-  $h_{ie}$
  - Similarly for common base  $h_{ib}$
  - for common collector :-  $h_{ic}$

- \*  $h_{12}$  :- Reverse voltage gain
  - for common emitter :-  $h_{re}$
  - common base :-  $h_{rb}$
  - common collector :-  $h_{rc}$

- \*  $h_{21}$  :- Forward current gain
  - Common emitter :-  $h_{fe}$
  - Common base :-  $h_{fb}$
  - Common collector :-  $h_{fc}$


- \*  $h_{22}$  :- o/p admittance
  - Common emitter :-  $h_{oe}$
  - Common base :-  $h_{ob}$
  - Common collector :-  $h_{oc}$

D-4.11.18

⇒ We have calculate current gain, voltage gain, input impedance and output impedance in different configuration of a transistor using H-parameters.

⇒ In most of the practical circuit we may use simplified Hybrid-model such an approximately model is justify because H-Parameter.

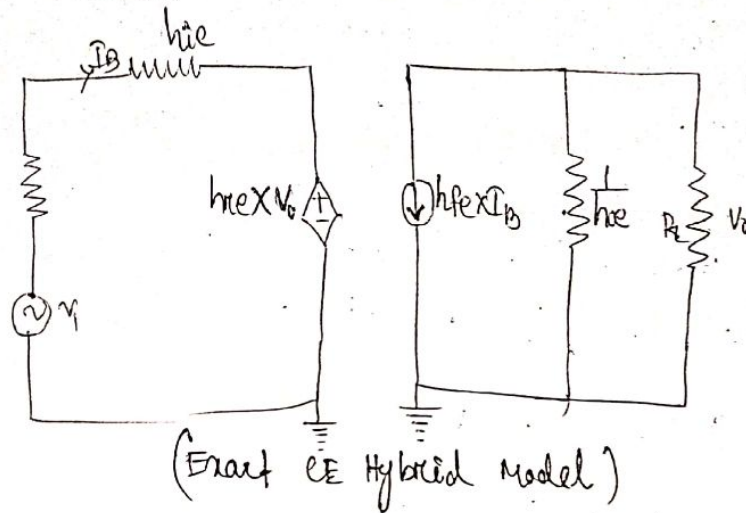⇒ Since CE configuration is most widely used it is taken for consideration.



⇒ We proceed to find simplified approximate and accurate version of this model.

⇒ From the figure the resistance  $(\frac{1}{h_{oe}})$  appears in parallel with load resistance  $R_L$ .

⇒ The collector current is given by; forward current gain  $\times$  input current  $(h_{fe} \times I_B)$

$$I_C = I_E R_L$$

$$\Rightarrow V_o = h_{fe} \times I_B \times R_L$$

⇒ According to magnitude of voltage generation in emitter circuit also get modified. It is given by;  $h_{ce} \times V_o$


$$= h_{ce} \times h_{fe} \times I_B \times R_L$$

Since  $h_{ce} \times h_{fe} \approx 0.01$

⇒ This voltage may be neglected in comparison with the voltage drop across  $h_{ie} = h_{ie} \times I_B$ , provided that  $R_L$  is not too large.

⇒ Thus it becomes possible to neglect parameter  $h_{oe}$

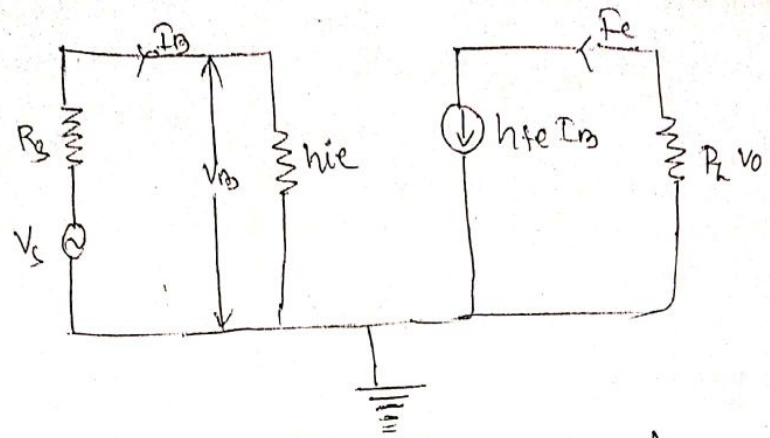
$h_{ce}$  in approximate CE hybrid model and use only remaining to other  $\pi$ -parameter ( $h_{fe}, h_{ie}$ )



(Approximate CE hybrid model)

Generalised approximate model:-

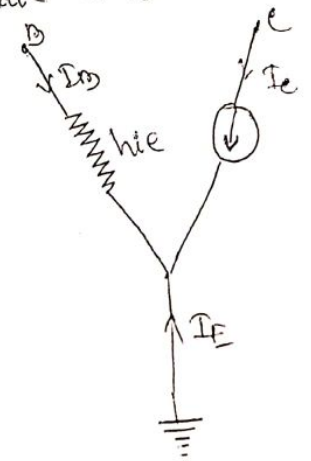⇒ The approximate CE h-model is re-derivation.




(Generalised CE hybrid model)

⇒ This model can be used for any configuration by shifting the appropriate terminal.

⇒ It is observed that the error in calculating  $Z_i, A_i, A_v, Z_o$  by the use of approximate model is less than 10%.

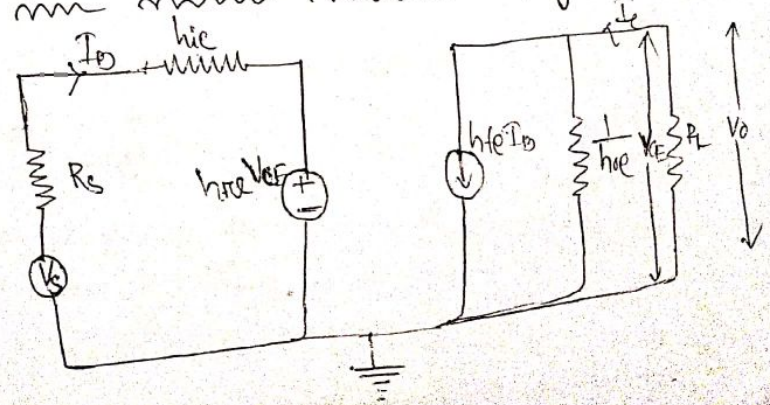Analysis of a transistor Amplifier using H-parameters:-



The hybrid eq<sup>n</sup> for this configuration is given by;

$$V_{BE} = I_{B_0} \times h_{ie} + V_{CE} h_{re} \quad \text{--- (1)}$$

Similarly,  $I_C = h_{fe} I_B + V_{CE} h_{oe} \quad \text{--- (2)}$

$$V_{CE} = -I_C R_L \quad \text{--- (3)}$$

(i) Current gain ( $A_{ic}$ ):-

The current gain is defined as the ratio of o/p current to the i/p current.

$$A_{ic} = \frac{I_C}{I_B} = \frac{-I_C}{I_B}$$

Substituting  $V_{CE}$  from eq<sup>n</sup> (3) in eq<sup>n</sup> (2) we get,

$$I_C = h_{fe} I_B - I_C R_L h_{oe}$$

$$\Rightarrow I_C + I_C R_L h_{oe} = h_{fe} I_B$$

$$\Rightarrow I_C (1 + R_L h_{oe}) = h_{fe} I_B$$

$$\Rightarrow \frac{I_C}{I_B} = \frac{h_{fe}}{1 + R_L h_{oe}}$$

$$A_{ic} = - \frac{I_C}{I_{B_0}}$$

$$\Rightarrow A_{ic} = - \left( \frac{h_{fe}}{1 + R_L h_{oe}} \right)$$

(ii) Input resistance ( $R_i$  /  $Z_i$ ):-

This is defined as the ratio of i/p voltage across the i/p terminal of an amplifier to the i/p current.

$$Z_i \text{ or } R_i = \frac{V_{BE}}{I_B}$$

Substituting the value of  $I_C$  from eq<sup>n</sup> (3) in eq<sup>n</sup> (2) we get,

$$I_C = h_{fe} I_B + V_{CE} h_{oe}$$

$$V_{CE} = -I_C R_L$$

$$\rightarrow I_e = -\frac{V_{ce}}{R_L}$$

$$I_e = h_{fe} I_b + V_{ce} h_{oe}$$

$$\rightarrow -\frac{V_{ce}}{R_L} = h_{fe} I_b + V_{ce} h_{oe}$$

$$\rightarrow -\frac{V_{ce}}{R_L} - V_{ce} h_{oe} = h_{fe} I_b$$

$$\rightarrow -V_{ce} \left( \frac{1}{R_L} + h_{oe} \right) = h_{fe} I_b$$

$$\rightarrow -\frac{V_{ce}}{I_b} = \frac{h_{fe}}{\frac{1}{R_L} + h_{oe}}$$

$$\rightarrow \frac{V_{ce}}{I_b} = - \left( \frac{h_{fe}}{\frac{1}{R_L} + h_{oe}} \right)$$

from eq (1)  $V_{be} = I_b h_{ie} + V_{ce} h_{re}$

$$\rightarrow \frac{V_{be}}{I_b} = \frac{I_b h_{ie}}{I_b} + \frac{V_{ce} h_{re}}{I_b}$$

$$\rightarrow \frac{V_{be}}{I_b} = h_{ie} + h_{re} \left( \frac{V_{ce}}{I_b} \right)$$

$$\rightarrow \frac{V_{be}}{I_b} = h_{ie} + h_{re} \left( -\frac{h_{fe}}{\frac{1}{R_L} + h_{oe}} \right)$$

$$\rightarrow \frac{V_{be}}{I_b} = h_{ie} - \frac{h_{re} h_{fe}}{\frac{1}{R_L} + h_{oe}}$$

$$Z_i \text{ or } R_i = h_{ie} - \frac{h_{re} h_{fe}}{\frac{1}{R_L} + h_{oe}}$$

(ii) Voltage gain ( $A_v$ ) :-

Voltage gain is defined as the ratio of o/p voltage to the i/p voltage.

$$A_v = \frac{V_{ce}}{V_{be}}$$

$$R_e \text{ or } Z_{ie} = \frac{V_{be}}{I_b}$$

$$\rightarrow V_{be} = I_b \times R_e$$

$$A_{ve} = \frac{V_{ce}}{I_b \times R_{ie}}$$

$$\Rightarrow A_{ve} = \left( \frac{V_{ce}}{I_b} \right) \times \frac{1}{R_{ie}}$$

$$\Rightarrow A_{ve} = \frac{-h_{fe}}{\frac{1}{R} \text{thoe}} \times \frac{1}{R_{ie}}$$

(ii) output resistance or impedance :-

The o/p resistance  $R_{oe}$  is obtained by setting  $V_{be}$  to zero  $R_L \rightarrow \infty$  and by driving o/p terminal from a generator from voltage  $V_{ce}$ .

The o/p resistance  $R_{oe} = \frac{\text{output voltage}}{\text{output current}}$

$$\Rightarrow R_{oe} = \frac{V_{ce}}{I_e}$$

from eqn (2)  $I_e = h_{fe} I_b + V_{ce} h_{oe}$

$$\Rightarrow \frac{I_e}{V_{ce}} = \frac{h_{fe} I_b}{V_{ce}} + \frac{h_{oe} \cdot V_{ce}}{V_{ce}}$$

$$\Rightarrow \frac{I_e}{V_{ce}} = \frac{h_{fe} \cdot I_b}{V_{ce}} + h_{oe}$$

$$\left. \begin{array}{l} V_{be} = 0 \\ R_L \rightarrow \infty \end{array} \right\} \text{from eqn (1)} \\ V_{be} = V_{ce} h_{re} + I_b h_{ie}$$

$$\Rightarrow 0 = V_{ce} h_{re} + I_b h_{ie}$$

$$\Rightarrow -V_{ce} h_{re} = I_b h_{ie}$$

$$\Rightarrow \frac{-V_{ce}}{I_b} = \frac{h_{ie}}{h_{re}}$$

$$\Rightarrow \frac{V_{ce}}{I_b} = -\frac{h_{ie}}{h_{re}}$$

$$\Rightarrow \frac{I_b}{V_{ce}} = -\frac{h_{re}}{h_{ie}}$$

$$\frac{I_c}{V_{ce}} = \frac{h_{fe} I_b}{V_{ce}} + h_{oe}$$

$$\Rightarrow \frac{I_c}{V_{ce}} = -\frac{h_{fe} \cdot h_{ie}}{h_{ie}} + h_{oe}$$

$$\Rightarrow \frac{I_c}{V_{ce}} = -\frac{h_{fe} \cdot h_{oe} + h_{oe} \cdot h_{ie}}{h_{ie}}$$

$$\Rightarrow \frac{V_{ce}}{I_c} = \frac{h_{ie}}{h_{oe} \cdot h_{ie} - h_{fe} \cdot h_{ie}}$$

$$\Rightarrow R_{oe} = \frac{V_{ce}}{I_c} = \frac{h_{ie}}{h_{oe} \cdot h_{ie} - h_{fe} \cdot h_{ie}}$$

$\Delta h = h_{ib} \cdot h_{ob} - h_{fb} \cdot h_{rb}$

characteristics	Common emitter	Common base	Common collector
Input impedance	$Z_i = h_{ie} - \frac{h_{fe} h_{ie}}{R_L + h_{oe}}$	$Z_{ib} = h_{ib} - \frac{h_{fb} h_{rb} R_L}{1 + h_{ob} R_L}$	$Z_{ic} = h_{ic} - \frac{h_{fc} h_{rc} R_L}{1 + h_{oc} R_L}$
Voltage gain	$A_{ve} = -\frac{h_{fe}}{R_L + h_{oe}} \cdot \frac{1}{R_{ie}}$	$A_{vb} = \frac{-h_{fb} R_L}{h_{ib} + \Delta h R_L}$	$A_{vc} = \frac{-h_{fc} R_L}{h_{ic} + \Delta h R_L}$
Current gain	$A_{ie} = -\frac{h_{fe}}{1 + h_{oe} R_L}$	$A_{ib} = \frac{-h_{fb}}{1 + h_{ob} R_L}$	$A_{ic} = -\frac{h_{fc}}{1 + h_{oc} R_L}$
Output impedance	$R_{oe} = \frac{h_{ie}}{h_{ie} \cdot h_{oe} - h_{fe} \cdot h_{ie}}$	$R_{ob} = \frac{R_S + h_{ib}}{R_S h_{ob} + h_{ib} h_{ob} - h_{fb} h_{rb}}$	$R_{oc} = \frac{R_S + h_{ic}}{R_S h_{oc} + h_{ic} h_{oc}}$

D-6-11-18

Multi stage transistor amplifier:-

- ⇒ When the voltage amplification or power gain of a single stage amplifier is insufficient to meet the requirement then multi stage transistor amplifier is used.
- ⇒ In multi stage amplifier in opp of the 1st stage is combined to the next stage <sup>through</sup> the coupling device. This process is called cascading.

⇒ A two stage amplifier connected in cascade



⇒ The over all gain of multi stage amplifier is equal to product of individual amplifier.

⇒ If  $A_v$  be the overall gain then  $A_v = A_{v1} \times A_{v2}$

⇒ The following are the purpose of coupling device :-

→ To transfer the A.C output of one stage to the i/p of next stage.

→ To block the d.c to pass from one stage to next stage

⇒ The four basic method of coupling are :-

(i) Resistance and capacitance coupling

(ii) Impedance coupling

(iii) transformer coupling

(iv) Direct coupling

(i) Resistance and capacitance coupling :-

⇒ The amplifier using R<sub>c</sub> coupling is known as R<sub>c</sub> coupled amplifier

⇒ In this coupling a resistance or capacitor are used as coupling device.

⇒ The capacitor connects the o/p of 1<sup>st</sup> stage to i/p of next stage. to pass A.C signal & to block D.C bias voltage.

(ii) Impedance coupling :-

⇒ Amplifier using this coupling is known as impedance coupled amplifier



→ This coupling <sup>network</sup> consists of inductance and capacitance. 41

(ii) Transformer Coupling:-

⇒ Amplifier using this coupling is known as Transformer coupled amplifier.

⇒ In this coupling transformer used as coupling device.

⇒ In this case there is capacitor is used as coupling device because the secondary of coupling transformer convey the a.c component directly.


(iii) Direct Coupling:-

⇒ Amplifier using this coupling is known as Direct Coupled device.

⇒ In this case the individual amplifier stage bias condition are show design that two stages may be directly connected without necessary dc isolation.

Point Thus the majority of transistor amplifier are of common emitter type. The resistance, capacitance network is most commonly used as coupling bet two stages.

RC-coupled transistor amplifier

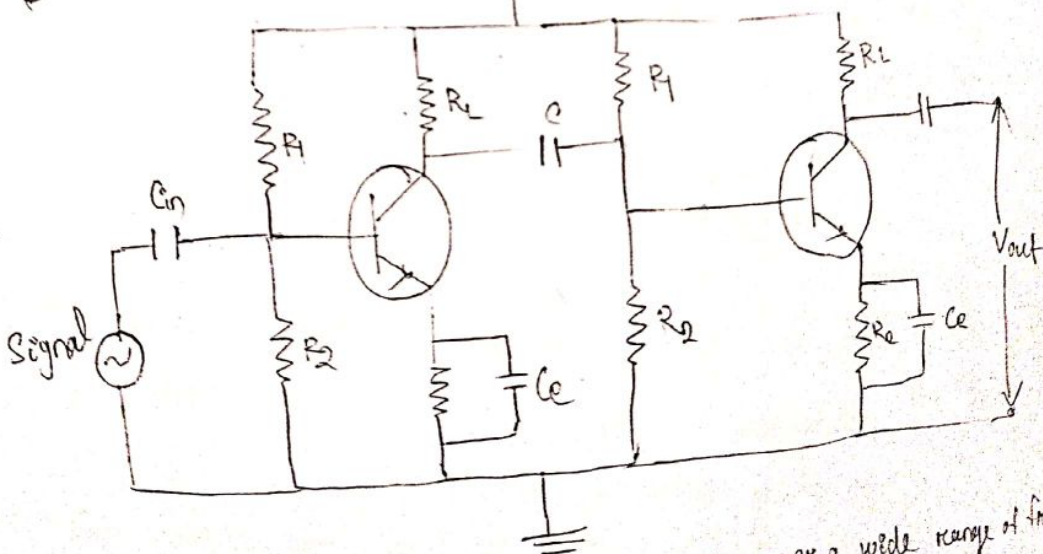

Application:- (i) They have excellent audio fidelity over a wide range of frequencies. (ii) widely used as voltage amplifier (iii) Due to poor impedance matching RC coupling is rarely used in final stage.

- ⇒ Fig. shows a two stage RC coupled amplifier using common emitter configuration.
- ⇒ The two transistors are identical & a common power supply  $V_{CC}$  is used.
- ⇒ The resistors  $R_1, R_2$  &  $R_E$  form the biasing and stabilization network.
- ⇒ The emitter bypass capacitor  $C_E$  offers low reactance path to signal.
- ⇒ The resistor  $R_L$  is used as load impedance.
- ⇒ The i/p capacitor  $C_{in}$  couples ac signal voltage to the base of transistor.
- ⇒ In absence of  $C_{in}$  the signal source will be in parallel with  $R_2$ .
- ⇒ The bias voltage of base will be changed.
- ⇒ Thus the  $f_c$  of  $C_{in}$  is to allow only ac ~~current~~ from signal source to flow into the i/p circuit.
- ⇒ The o/p of the 1<sup>st</sup> stage is coupled to the i/p of 2<sup>nd</sup> stage through a coupling capacitor  $C_c$ .
- ⇒ This allows ac signal to pass through it and blocks dc components.
- ⇒ When ac signal is applied to the base of 1<sup>st</sup> transistor it appears across connected load  $R_L$  in the amplified form.
- ⇒ Through coupling capacitor  $C_c$  the amplified signal is transferred to the next stage of amplifier this is further amplified next stage.
- ⇒ So cascaded stage amplify the signal and overall gain is increased.

Analysis:-

In the analysis of coupled amplifier the following approximations are made.

(i)  $h_{ie}$  is so small that voltage source  $h_{ie} i_b$  can be neglected.


(ii)  $R_{in}$  is so large so it is open circuit.

(iii) The reactance of  $C_c$  for any given  $f$  is so small

that the parallel combination  $R_{in} \parallel C_c$  can be effectively

considered as short cut.

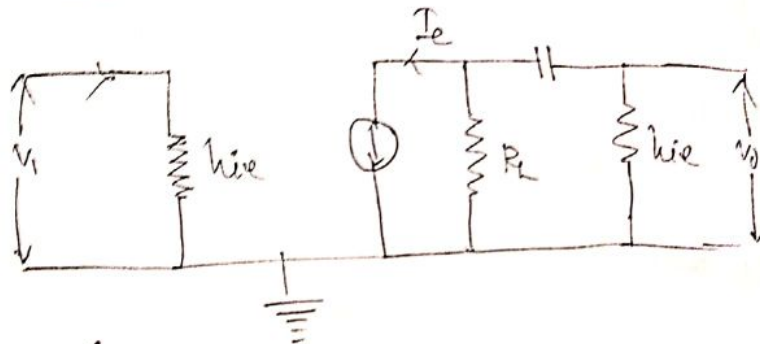
(iv) The bias resistors  $R_1$  and  $R_2$  are usually large as compared to  $h_{ie}$



(Simplified equivalent circuit of RC coupled amplifier)

Frequency response curve and bandwidth:-

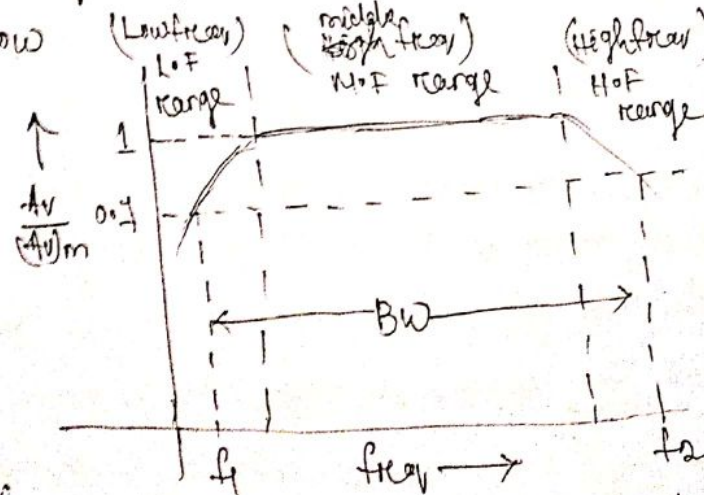The freq. response curve of RC coupled amplifier is shown below



(frequency response curve of RC coupled amplifier)

⇒ It is obvious from analysis of  $R_e$  coupled amplifier that the gain of the amplifier is independent of freq. but mid-freq (MF) range but decreases at both high and low freq.

⇒ At low frequency the reactance of coupling capacitor ( $\frac{1}{\omega C_c}$ ) is quite high. Hence a very small part of a signal passes from one stage to the next stage.

⇒ At low freq. the reactance of  $C_e$  is comparable to the resistance  $R_e$ .


⇒ So the bypass action of this capacitor is no longer as good as at mid & high freq. range. Hence it reduces the voltage.

⇒ At high freq. the capacitor  $C_{bc}$  bet<sup>n</sup> base & collector causes the o/p with i/p.

⇒ As a result -ve feedback takes place. Hence gain decreases.

⇒ Beside inter electrode capacitance there are wiring capacitance  $C_{w1}, C_{w2}$  and o/p capacitance  $C_o$ .

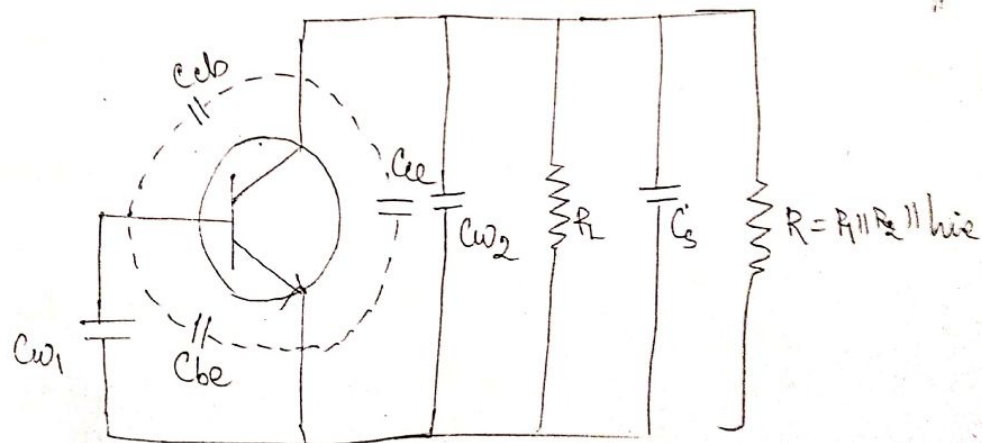⇒ The effect of o/p circuit can be expressed by a single capacitance  $C_s$ .  $C_s = C_e + C_{w1} + C_o$



(output section of high freq.)

Band width:-

⇒ The difference of upper cut-off freq. and lower cut-off freq.

is called as band width.

$$BW = f_2 - f_1$$

⇒ when the BW is multiplied <sup>with</sup> the gain at mid freq. this is called as gain band width (GBW)

⇒ we know the power is square of voltage. Thus the power of at the cut-off freq become  $\frac{1}{2}$  of the power of the mid freq

because

$$\frac{(AV)_L}{(AV)_m} = \frac{1}{\sqrt{2}}$$

D-8.11.18

Transformer Coupled Circuit Amplifier:-

⇒ Here a coupling transformer is used to feed the o/p of 1<sup>st</sup> stage to the i/p of the next stage.

⇒ The collector load is replaced by primary winding of the transformer.

⇒ The secondary is connected bet<sup>n</sup> base of 2<sup>nd</sup> stage and voltage divider i.e. the secondary of transformer gives i/p to the next stage.

⇒ The transformer T<sub>2</sub> is the o/p transformer. The other components are same as in RC coupled amplifier.

⇒ It should be noted that, there is no coupling capacitor.


⇒ When i/p is applied to the base of transistor T<sub>1</sub> it is amplified and appears across the primary transformer T<sub>1</sub>.

⇒ By magnetic induction it is passed to the secondary.

Now the o/p is applied to the base of transistor T<sub>2</sub>.

⇒ The amplified o/p appears across the primary of transformer T<sub>2</sub>.

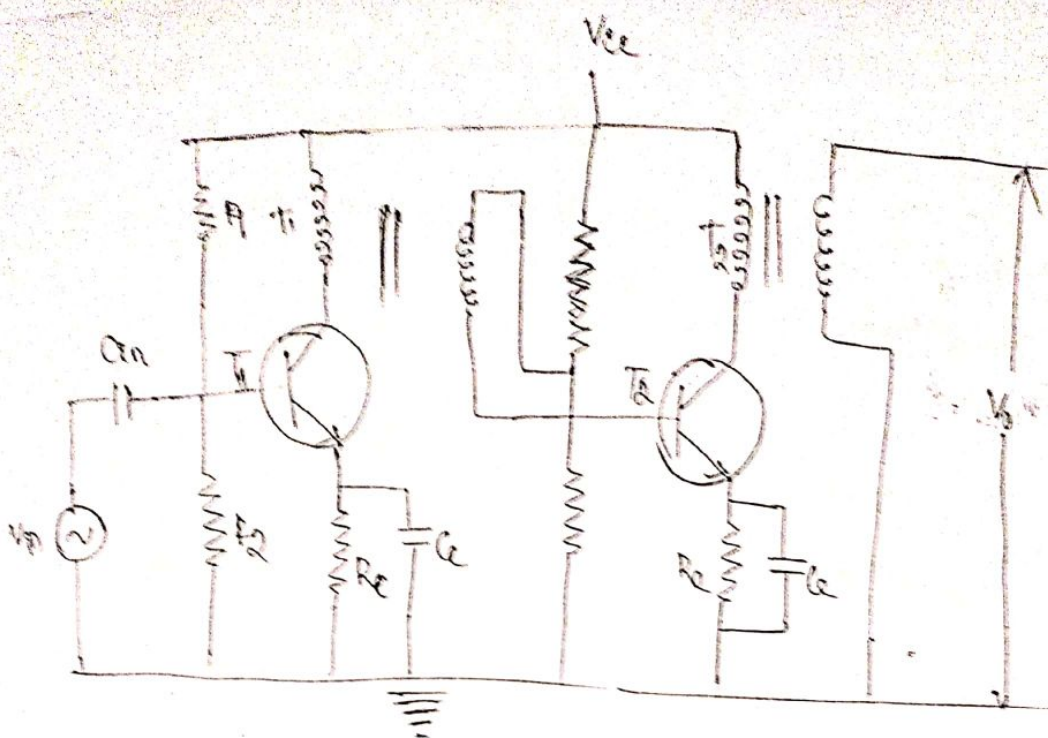⇒ The circuit diagram of two stage transformer coupled amplifier is shown below.



### Advantage:-

- ⇒ The absence of resistor  $R_c$  in the collector circuit eliminates the unnecessary power loss in the resistor.
- ⇒ The operation of transformer coupled system is more efficient because of low ac resistance of primary ~~winding~~ <sup>collector out-</sup> connection.
- ⇒ Due to excellent impedance matching the transformer <sup>coupling</sup> provides higher gain.

### Disadvantages:-

- ⇒ It has poor freq. response.
- ⇒ The ckt transformer is bulky & costly.

### Negative feedback in Amplifier:-

- ⇒ When a part of fraction of o/p is combined to the i/p feedback is said to exist.
- ⇒ Thus a process of combining a fraction of o/p energy back to the i/p is known as feedback.
- ⇒ If the net effect of feedback is to reduce the magnitude of o/p signal is called as -ve feedback or regeneration.
- ⇒ The -ve feedback reduces the gain of amplifier.

## Advantage of -ve feedback:-

44

- ⇒ Stabilization of gain reduction in distortion.
- ⇒ Reducing in noise.
- ⇒ Increase in i/p impedance.
- ⇒ Decrease in o/p impedance.
- ⇒ Increase in range of uniform amplification.

## Positive feedback:-


- ⇒ If the net effect of feedback is to increase the magnitude of i/p signal it is called as "positive direct or regenerative".
- ⇒ The +ve feedback has the disadvantage of increased distortion and instability.
- ⇒ So +ve feedback is seldom used in amplifiers.

## General theory of feedback:-

The feedback amplifiers are classified into two general classes:-

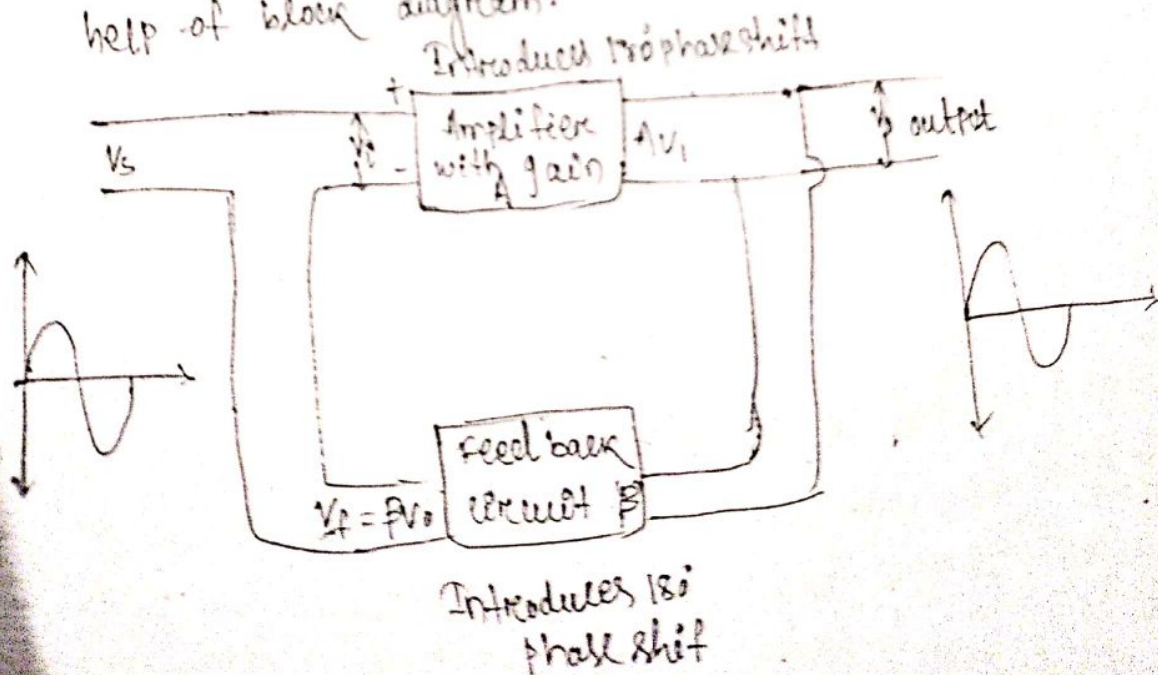- (i) voltage feedback
- (ii) current feedback

The general theory of feedback can be understood with the help of block diagram.



⇒ The feedback amplifiers have two parts :-

(1) Amplifier

(2) feedback circuit

⇒ The feedback circuit usually consists of resistors.

⇒ This returns a fraction of o/p voltage back to the i/p.

⇒ Let 'A' be the gain of amplifier. This is the gain of amplifier

⇒ The feedback network extracts a voltage  $V_f = \beta V_o$  from the o/p  $V_o$  of the amplifier.

⇒ The voltage is added or subtracted from the signal voltage  $V_s$ .

$$V_i = V_s + V_f \text{ (for +ve feedback)}$$

$$V_i = V_s + \beta V_o$$

Similarly,

$$V_i = V_s - V_f \text{ (for -ve feedback)}$$

$$V_i = V_s - \beta V_o$$

⇒ Consider in the case of -ve feedback the o/p  $V_o$  must be equal to i/p voltage ( $V_s - \beta V_o$  multiplied by gain 'A' of amplifier).

$$(V_s - \beta V_o) A = V_o$$

$$\Rightarrow AV_s - A\beta V_o = V_o$$

$$\Rightarrow AV_s = V_o + A\beta V_o$$

$$\Rightarrow AV_s = V_o (1 + A\beta)$$

$$\Rightarrow \boxed{\frac{V_o}{V_s} = \frac{A}{1 + A\beta}}$$

⇒ Let  $A_f$  be the overall gain of the amplifier this is defined as the ratio of o/p voltage  $V_o$  to the applied voltage  $V_s$ .

$$A_f = \frac{\text{output voltage}}{\text{i/p signal voltage}} = \frac{V_o}{V_s}$$



we have  $A_f = \frac{A}{1 + A\beta}$  (for -ve feed back)

similarly,  $A_f = \frac{A}{1 - A\beta}$  (for +ve feed back)

we consider the three cases:-


- (i) for -ve feed back,  $A_f < A$
  - (ii) for +ve feed back,  $A_f > A$
  - (iii) If  $A\beta = 1$ , then  $A_f = \infty$
- This is only possible when  $\angle \beta$  is zero.

Negative feed back ext:-

⇒ when the feed back signal is out of phase with the i/p signal and thus opposes it then the feed back is known as "-ve feed back".

⇒ The -ve feed back amplifier introduces phase shift of 180° in the o/p wave

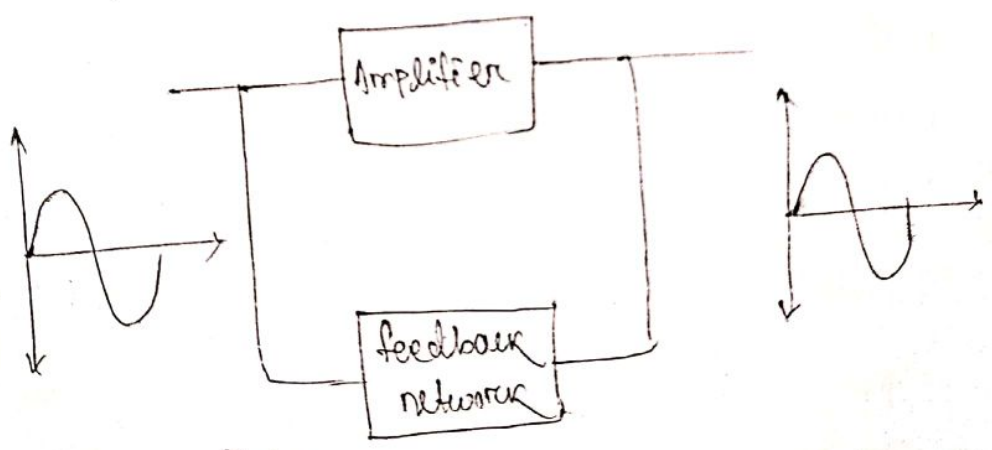⇒ While the feed back amplifier introduces no phase shift, i.e. the feed back network is designed such a way that it does not introduce any phase shift.



⇒ -ve feed back amplifier is a method of feeding a portion of the o/p amplifier o/p energy back to the i/p of the amplifier

There are two type of -ve feed back ext  
voltage feed back

### voltage feedback:-

→ In this method the voltage feedback to the i/p of the amplifier is a portion of the o/p voltage.

→ This is further classified into two types:-

(i) voltage series feedback

(ii) voltage shunt feedback

### negative current feedback:-

In this method the voltage feedback to the i/p of the amplifier is proportional to the o/p current.

It is further classified into two parts:-

(i) current series feedback

(ii) current shunt feedback

### POWER AMPLIFIER:-

→ The power amplifiers are large signal amplifiers which raise the power level of the signal.

→ The power amplifier may also be defined as a device which converts DC power to AC power whose action is controlled by the i/p signal.

→ Power amplifier takes power from DC power supply connected to o/p circuit & converts it into useful AC signal power.

→ The DC power is distributed acc. to the relation

$$DC \text{ power } i/p = AC \text{ power } o/p + \text{losses}$$

→ Power amplifiers divided into two parts:-

(i) audio power amplifier

(ii) radio power amplifier

Audio power amplifiers

⇒ The audio power amplifier raise the power level of signal that have audio freq. range (20 Hz - 20 kHz).  
 ⇒ They are also known as small signal power amplifier.

Radio Amplifiers

⇒ Radio amplifier or tuned power amplifier raise the power level of the signal that have radio freq. range (5 kHz - 300 MHz).  
 ⇒ They are also known as large signal power amplifier.

on the basis of mode of operation the portion of i/p cycle during which collector current flow the power amplifier may be classified as:-

- (i) class-A power amplifier
- (ii) class-B power amplifier
- (iii) class-C power amplifier

(i) class-A power amplifier:-

When the collector current flow at all time during the full cycle of signal the power amplifier is known as class A power amplifier.

(ii) class-B power amplifier:-

When the collector current flow only during the half cycle of the i/p signal the power amplifier is known as class B power amplifier.

(iii) class-C power amplifier:-

When the collector current flow for less than half cycle of the i/p signal the power amplifier is known as class C power amplifier.

difference bet<sup>n</sup> voltage amplifiers and power amplifiers:-

voltage amplifiers:-

⇒ The aim of voltage amplifier is to raise the voltage level of the signal.

⇒ The voltage amplifier is given by;  $A_v = \beta \left( \frac{R_c}{R_{in}} \right)$

The voltage amplifier having following characteristics:-

- The transistor with high  $\beta$  should be used.
- The i/p resistance  $R_{in}$  should be low.
- Collector load should be high
- They are used for small signal voltage.

Power amplifier:-


⇒ The aim of power amplifier is to raise the power level of the signal.

⇒ The power amplifier have following characteristics:-

- The transistor with comparatively <sup>low</sup>  $\beta$  is used.
- In order dissipate heat produced in transistor during operation
- Collector resistance made low
- Transformer coupling is used.

<u>Characteristics</u>	<u>voltage amplifier</u>	<u>power amplifier</u>
$\beta$	high	low
$R_c$	high	low
i/p voltage	low	high
o/p impedance	high	low
Coupling	RC coupled amplifier	transformer coupling

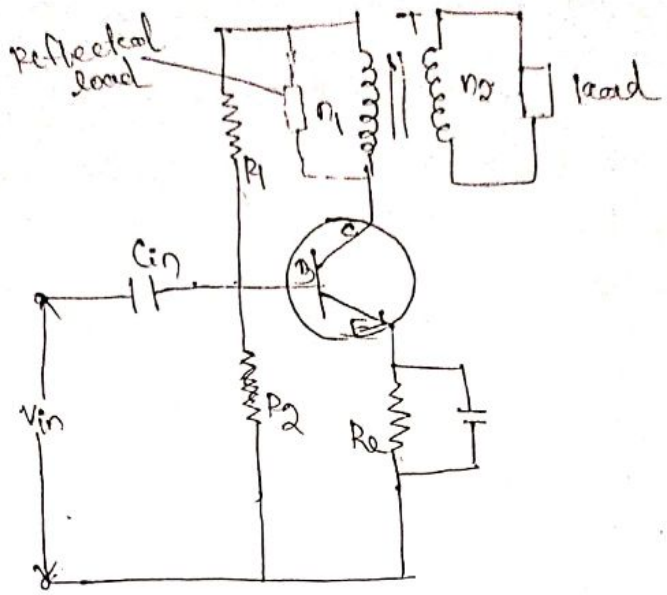Class A Power amplifier (transformer coupled):- 47



ID-90.11.18

- ⇒ R1 and R2 provide a potential divider arrangement for forward biasing emitter base junction, of the power transistor.
- ⇒ The RE is emitter resistor for bias stabilisation CE is bypass capacitor, RE to prevent AC voltage.
- ⇒ The capacitor Cb blocks any DC from the previous stage. Input signal from pre-amplifier is applied to the i/p terminal.
- ⇒ T is the stepdown transformer. The high impedance primary of the transformer is connected to high impedance of the collector circuit.
- ⇒ The low impedance secondary is connected to load.

Transformer impedance matching:-

- ⇒ Let RL is the load connected in secondary of a transformer
- ⇒ The reflected load in the primary of the transformer RL'
- ⇒ N1 and N2 are the numbers of turns in primary and secondary respectively-
- ⇒ Let V1 & V2 be the primary and secondary voltage and I1 and I2 primary & secondary current respectively

⇒ We know  $\frac{V_1}{V_2} = \frac{n_1}{n_2}$  and  $\frac{I_2}{I_1} = \frac{n_1}{n_2}$

$$V_1 = \frac{n_1}{n_2} \times V_2 \quad \text{and} \quad I_2 = \frac{n_1}{n_2} \times I_1$$

$$\Rightarrow I_1 = \frac{n_2}{n_1} \times I_2$$


$$\frac{V_1}{I_1} = \frac{\frac{n_1}{n_2} \times V_2}{\frac{n_2}{n_1} \times I_2}$$

$$\Rightarrow \frac{V_1}{I_1} = \frac{n_1^2}{n_2^2} \times \frac{V_2}{I_2}$$

$$\Rightarrow R_L' = \left(\frac{n_1}{n_2}\right)^2 \times R_L$$
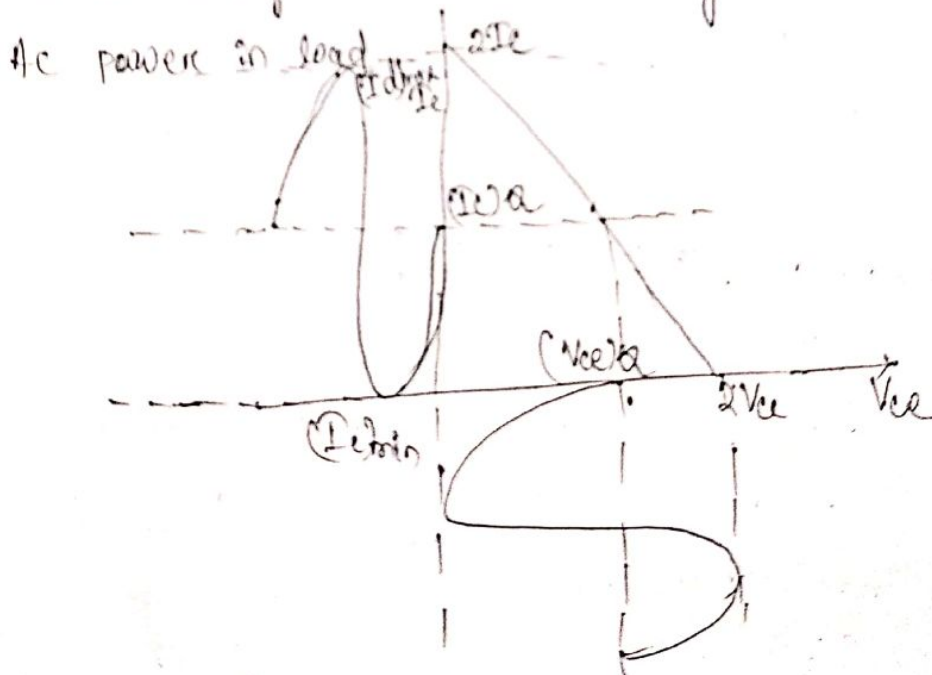
### Circuit operation:-

- ⇒ When ac signal is applied the collector current fluctuates
- ⇒ The operating point Q moves up and down the load line.
- ⇒ The collector voltage varies in opposite phase to the collector current.
- ⇒ The variation of collector voltage appears across the primary transformer.
- ⇒ The a.c voltage induced in secondary which is across



(output voltage of circuit wave form)

→ The power loss in primary transformer is negligible small because its resistance is very small.

→ Under this condition  $(P_{in})_{dc} = (P_{in})_{ac} = I_{CQ} V_{CC}$

→ Under max<sup>m</sup> capacity of a class-A amplifier voltage swing bet<sup>n</sup>  $V_{CE_{max}}$  to zero and the current from  $(I_C)_{max}$  to zero.

$$V_{rms} = \frac{1}{\sqrt{2}} \left\{ \frac{(V_{CE})_{max} - (V_{CE})_{min}}{2} \right\}$$

$$= \frac{1}{\sqrt{2}} \left\{ \frac{2V_{CC}}{2} \right\}$$

$$I_{rms} = \frac{1}{\sqrt{2}} \left\{ \frac{(I_C)_{max} - (I_C)_{min}}{2} \right\}$$

$$= \frac{1}{\sqrt{2}} \left\{ \frac{2I_{CQ}}{2} \right\}$$

$$= \frac{I_{CQ}}{\sqrt{2}}$$

$$\text{Power o/p} = V_{rms} \times I_{rms}$$

$$= \frac{V_{CC}}{\sqrt{2}} \times \frac{I_{CQ}}{\sqrt{2}}$$

$$= \frac{V_{CC} \cdot I_{CQ}}{2}$$

$$\text{Collector efficiency} = \frac{(P_o)_{out}}{(P_{in})_{dc}} \times 100$$

$$= \frac{V_{CC} \cdot I_{CQ}}{2} \times 100$$

$$= \frac{V_{CC} \cdot I_{CQ}}{V_{CC} \cdot I_{CQ}} \times 100$$

$$= \frac{1}{2} \times 100$$


$$= 50\%$$

In practical case the efficiency of power amplifier is less than 50%.

D-10-11-18

Class-A push pull power amplifiers -

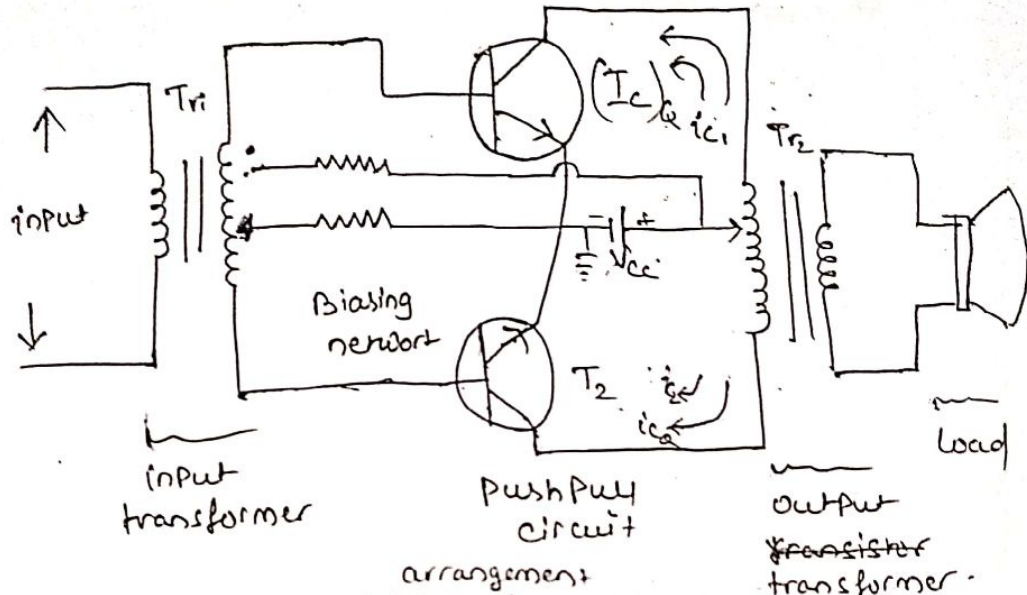The distortion introduced by non-linearity of a dynamic transfer characteristics



- ⇒ In Push Pull amplifier, two identical transistors  $T_1$  &  $T_2$  are used. The emitter terminals of two transistors are connected together the input signal is applied to the inputs of the two transistors through center tap transformer ( $T_{r1}$ )
- ⇒ This transformer provides opposite polarity signal of the two transistor input
- ⇒ The collector of the both transistors are connected to the primary of the output transformer ( $T_{r2}$ ) This transformer is also centre tap
- ⇒ The collector of both transistors are connected to supply  $V_{cc}$  through primary of output transformer
- ⇒ The resistor  $R_1$  &  $R_2$  provides the biasing arrangement
- ⇒ The load (a loudspeaker) is connected across the secondary of output transformer
- ⇒ The turn ratio of the output transformer is chosen in such a way that the load is well matched with the O/P impedance of trans.



So maximum power is delivered to load by the amplifier

### Advantage

- ⇒ Even harmonics are absent in the output
- ⇒ High AC O/P Power
- ⇒ The effect of Ripple voltage contain in Power Supply due to inadequate

### Disadvantage

- ⇒ Two identical transistor are required
- ⇒ Centre tap transformer is required.

## CLASS B : PUSH PULL POWER AMPLIFIER

We have seen that class A Push Pull Power amplifier reduces the harmonic distortion but the conversion efficiency is only 50%. To increase the efficiency class 'B' Push Pull amplifier is used.

⑧ Overall efficiency of class B Push Pull amplifier:

$$\text{Power input } (P_{in})_{dc} = V_{cc} \times I_{dc}$$

$$\text{we know } I_{dc} = \frac{(I_c)_{max}}{\pi}$$

$$(P_{in})_{dc} = \frac{V_{cc} \times (I_c)_{max}}{\pi}$$

$$\text{Rms value of collector current} = \frac{(I_c)_{max}}{\sqrt{2}}$$

$$\text{Rms value of voltage} = \frac{V_{cc}}{\sqrt{2}}$$

$$P_{out} = (P_o)_{ac} = \frac{1}{2} \times \frac{V_{cc}}{\sqrt{2}} \times \frac{(I_c)_{max}}{\sqrt{2}}$$

$$= \frac{V_{cc} \times (I_c)_{max}}{2 \times 2}$$

$$= \frac{V_{cc} \times (I_c)_{max}}{4}$$

$$\eta = \frac{\text{Output Power}}{\text{Input Power}} = \frac{P_{out}}{(P_{in})_{dc}}$$

$$= \frac{V_{cc} \times (I_c)_{max}}{4} \times \frac{\pi}{V_{cc} \times (I_c)_{max}}$$

$$= \frac{\pi}{4}$$


$$= \frac{\pi}{4}$$

$$= 0.785 \times 100$$

$$= 78.5\%$$

Class A Push Pull = 50%  
 Class B Push Pull = 78.5%

Note

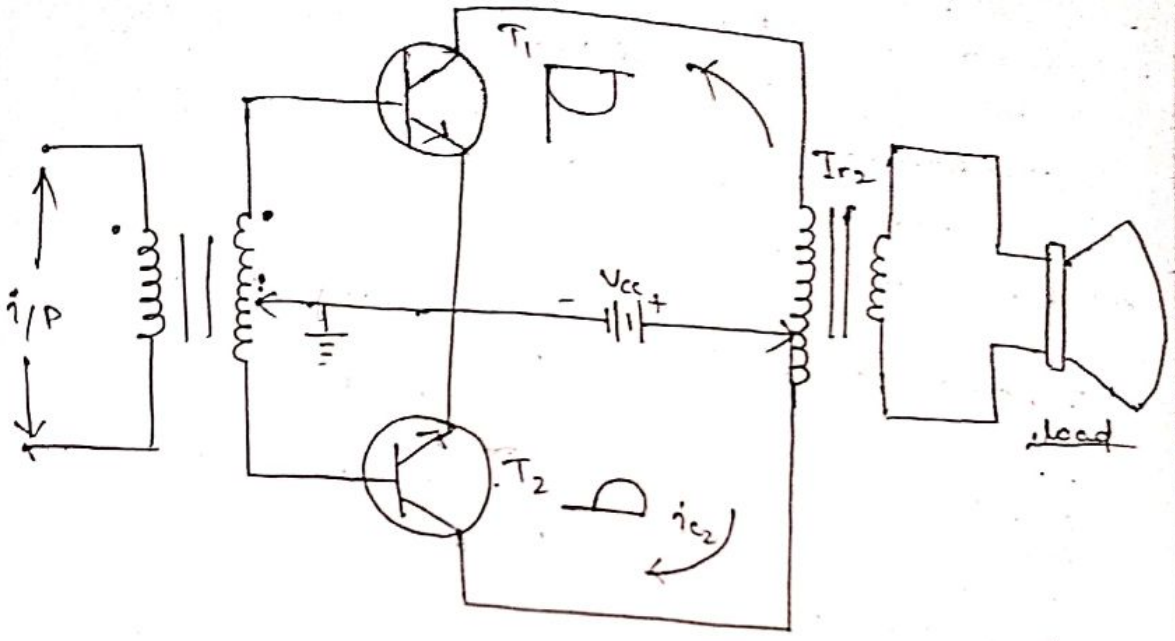

Class B Push-Pull amplifier


- The circuit arrangement of Class B Push Pull amplifier is same as that of class A Push Pull amplifier except that transistors are biased at cut off. This is done by providing zero bias on the base of each transistor
- By connecting the base and emitter together
- As shown in fig. the bases of two CE connected identical transistors have been connected to the opposite end of secondary of the input transformer ( $T_{r1}$ ) & collector ends to the primary of the output transformer ( $T_{r2}$ ). In order to get balanced circuit the emitters of the transistors are connected to the center tap of the secondary of transformer ( $T_{r1}$ ) &  $V_{cc}$  is connected to the center tap on the primary transformer ( $T_{r1}$ ). The two bases have been earthed.

Advantage

- ⇒ It's efficiency is greater than class A push pull amp
- ⇒ High AC output power

Disadvantage

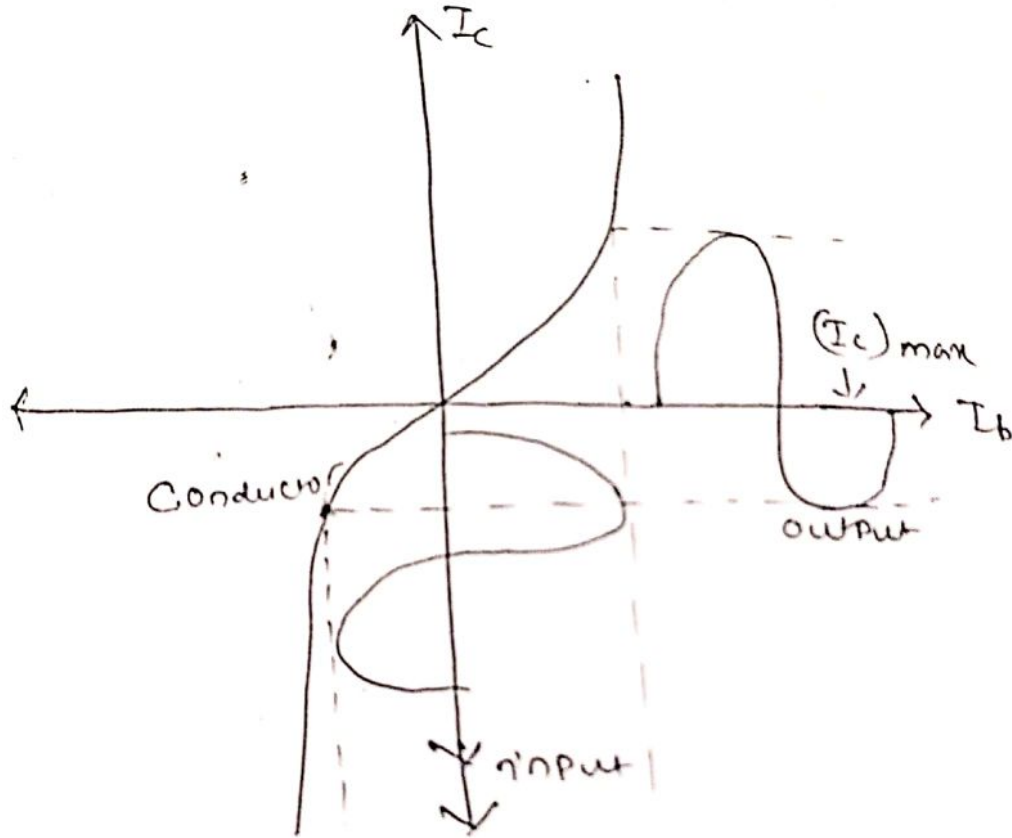The disadvantage of class B is same as class A.



Output wave form of class B push pull amplifier